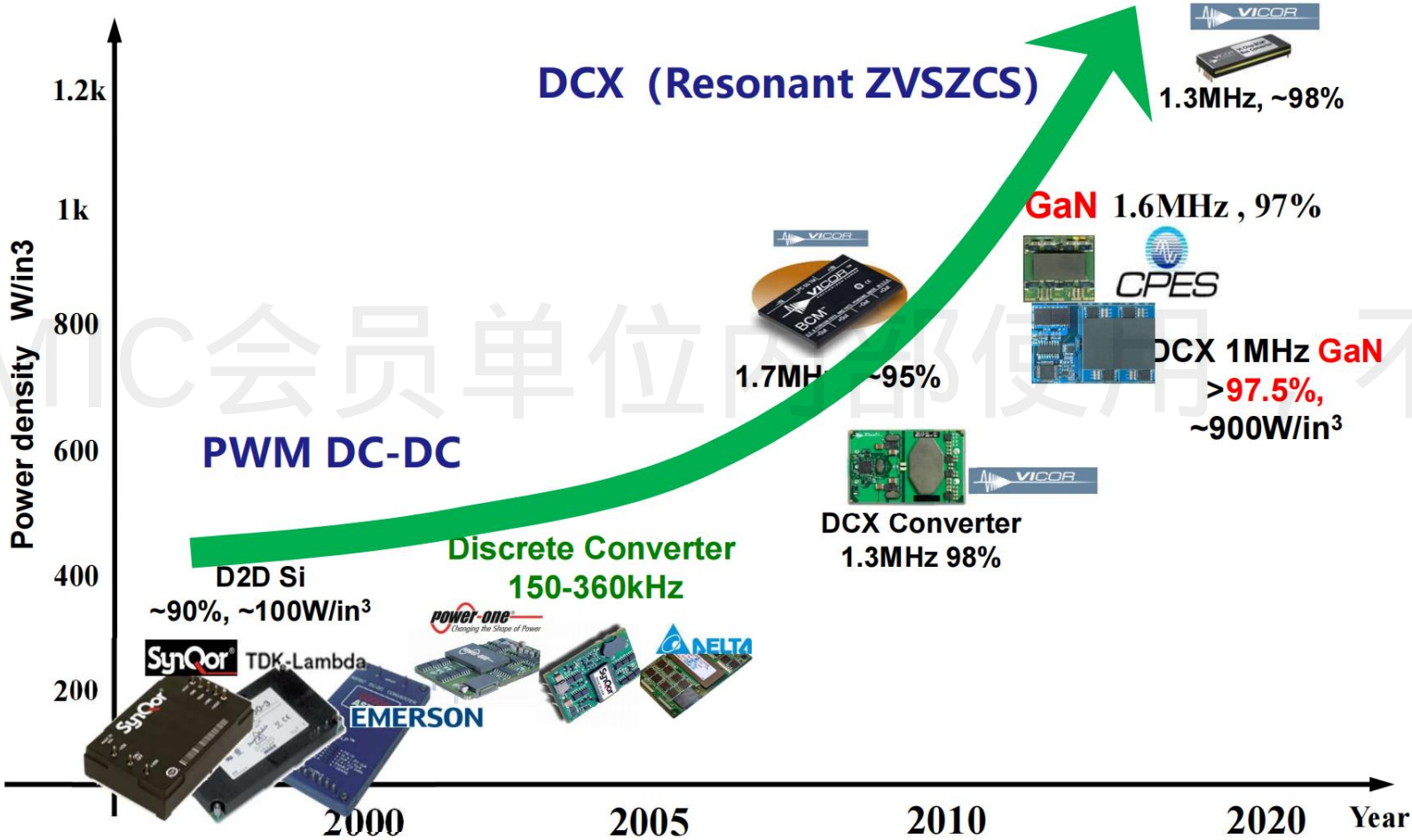


High Efficiency High Power Density Cellular 380V-12V DCX Using Low NFoM Devices

Xinke Wu Ph. D



Trends for Isolated DC/DC Converters




Popular Topology for MHz DCX



1.3MHz, ~98%



GaN

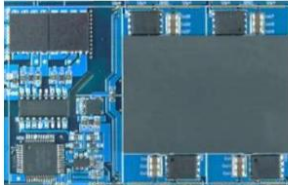


DCX 1MHz GaN
4 Layer PCB
97.5%, 900W/in³
(2016)



48V-12V
1MHz, >98%
(2019)




- LC Resonant
- Matrix Transformer

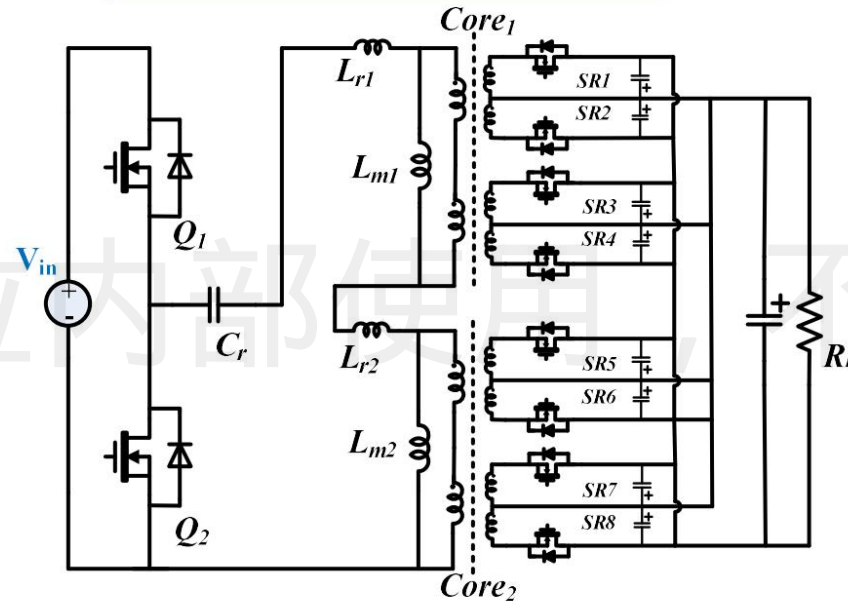



- ☺ ZVS on
- ☺ ZCS off
- ☺ Without reverse recovery

Does fully soft switching achieve high efficiency easily at MHz?

Density Comparison among DCXs

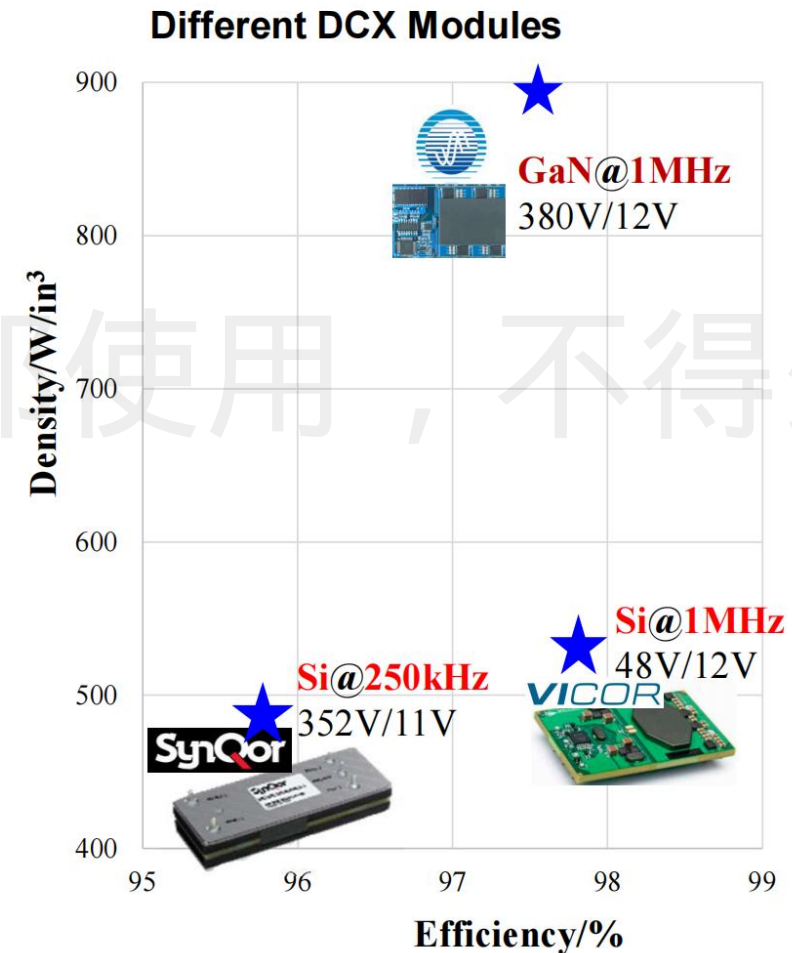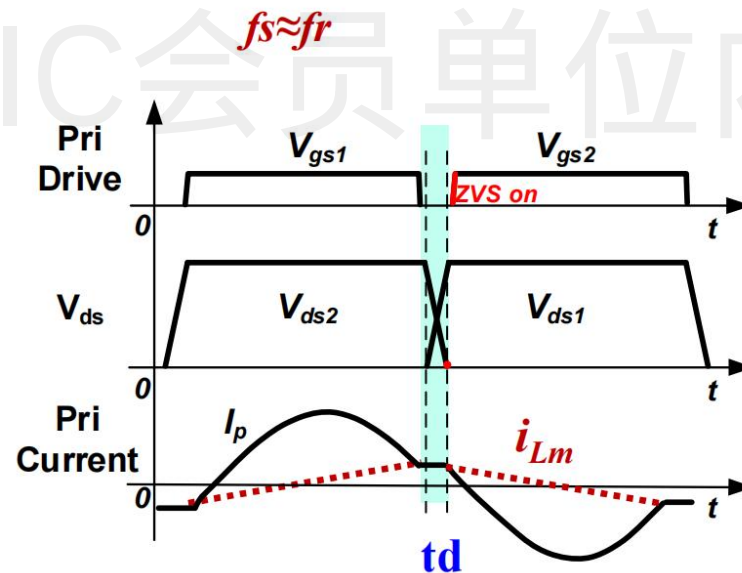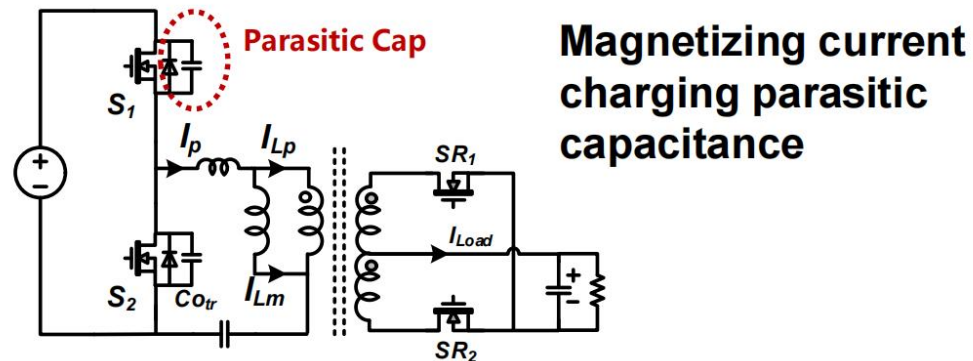


Primary Conduction Loss Model of DCXs

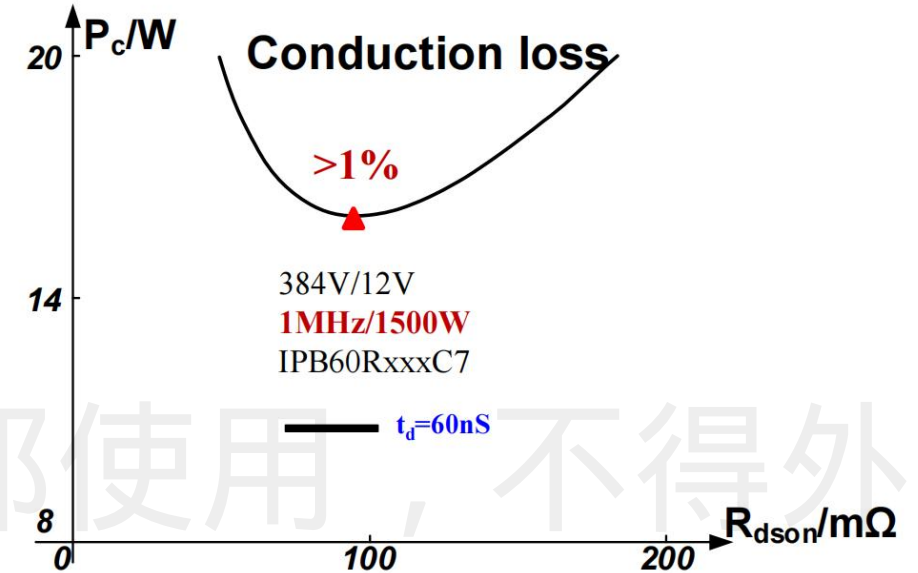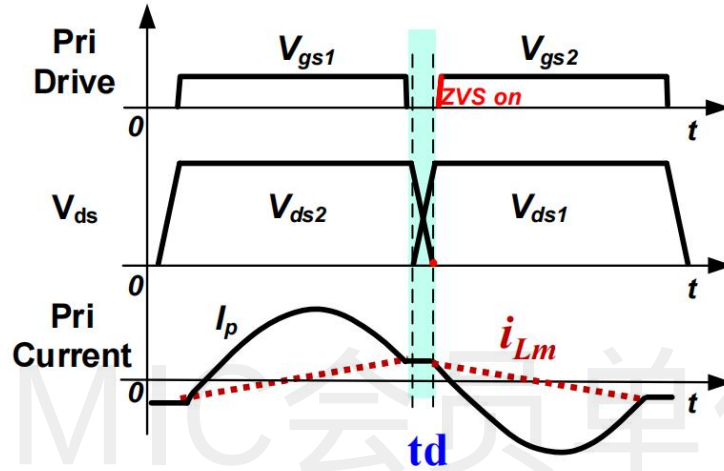

$$P_c(R_{dson}) = A * \frac{1}{R_{dson}} + B * R_{dson}$$

A and B: **Const.** $A = \frac{8n_T^2 V_o^2 T_r * NFoM^2}{t_d^2 T_s}$ $B = \frac{\pi^2 I_o^2 T_s}{8n_T^2 T_r}$

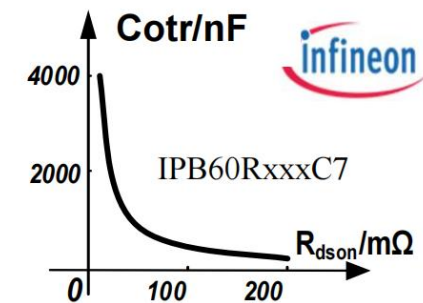Min. Loss: $P_c(R_{dson}) \geq 2\sqrt{AB} = P_{cmin} = \frac{2\pi V_o I_o * NFoM}{t_d}$




$$NFoM = R_{dson} * C_{otr}$$


Series-connected low NFoM devices

Low $V_{(BR)DSS}$ = Low NFoM
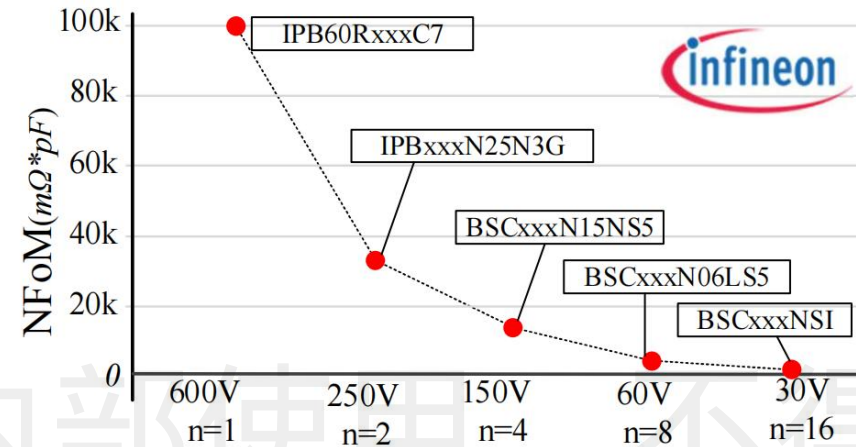
$$P_{Cmin} = \frac{2\pi * P_o * NFoM}{t_d}$$



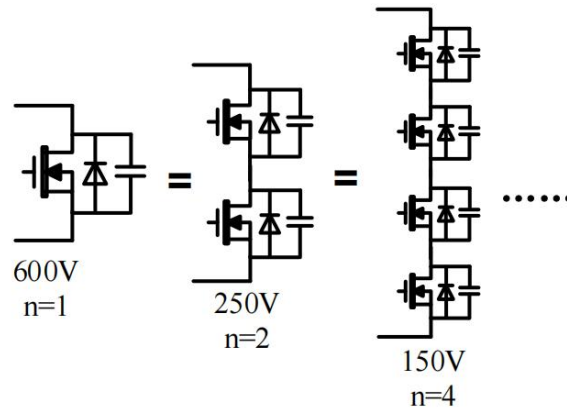Series-connected low $V_{(BR)DSS}$ devices




$$NFoM = (\cancel{n} R_{dson}) \cdot \frac{C_{otr}}{\cancel{n}}$$

Conduction loss depends to single low voltage device


Xinke Wu, Hongbo Shi, "High Efficiency High Density 1 MHz 380–12 V DCX With Low FoM Devices" IEEE TIE 2020. pp1648-1656




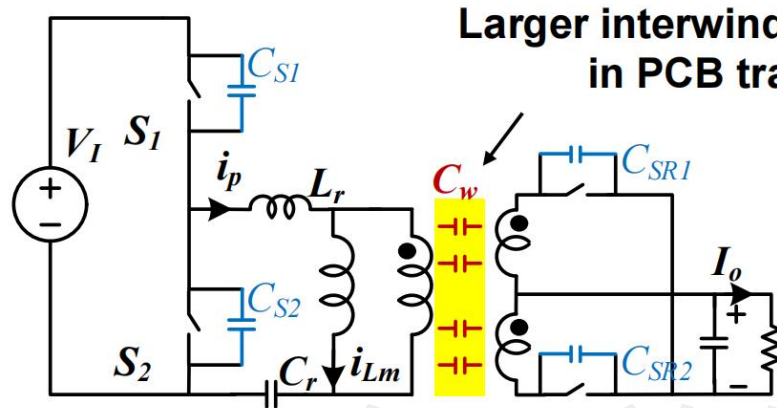
Interwinding Capacitance Sinking Magnetizing Current in PCB Transformer



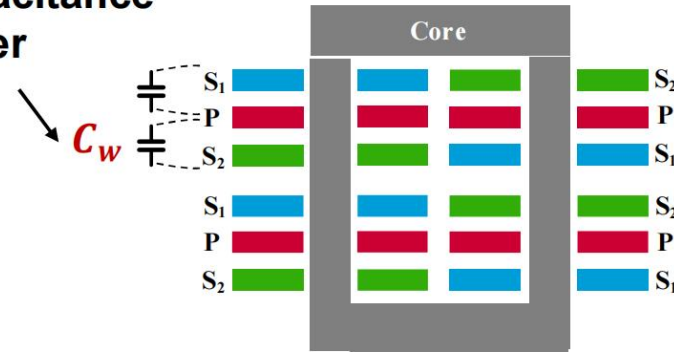Larger interwinding capacitance in PCB transformer



Simplified

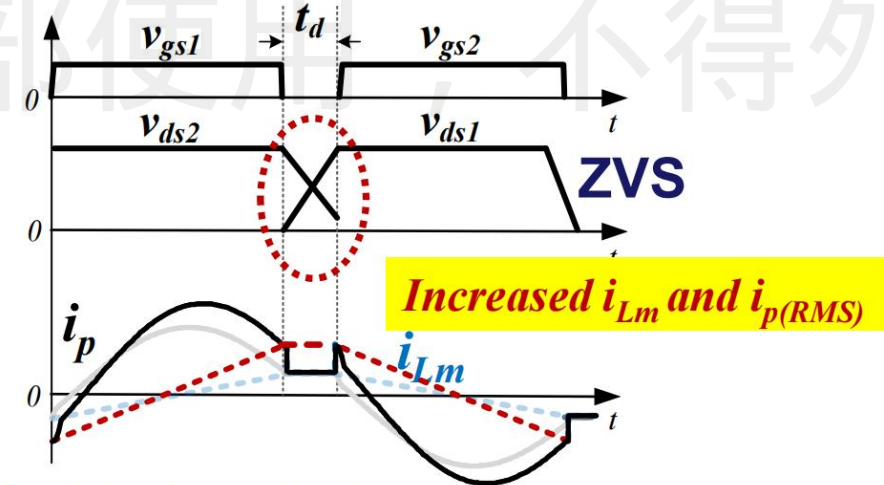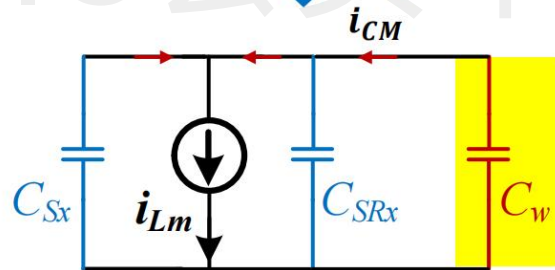


Larger magnetizing current for ZVS is Needed

D. Fu, S. Wang, P. Kong, etc., "Novel Techniques to Suppress the Common-Mode EMI Noise Caused by Transformer Parasitic Capacitances in DC-DC Converters," in IEEE TPEL, Nov. 2013,

Larger Magnetizing Current Leads to Higher Eddy Current Loss in Windings


■ Conventional SRC

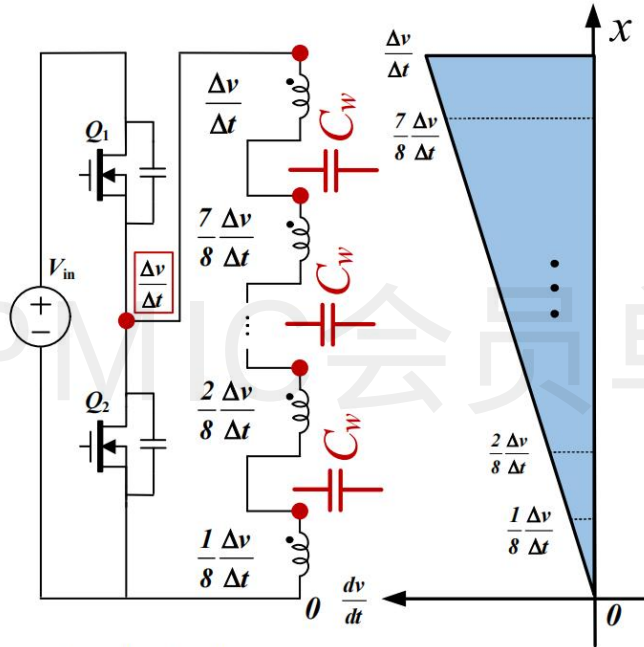


Δv : Input voltage
 Δt : Dead time

$$i_{CW} = 16C \cdot \frac{\Delta v}{\Delta t}$$

higher
magnetizing
current

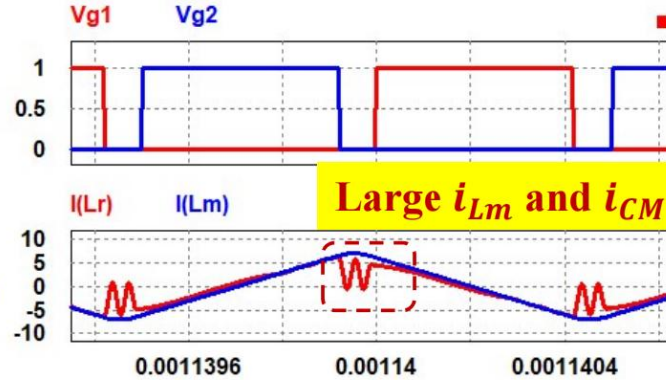


H field distribution 380V/12V DCX

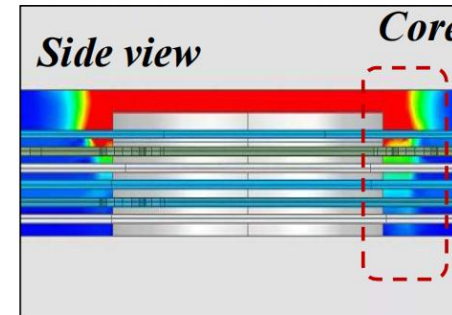


Total Winding loss $\approx 5.4W$

@ $I_o=0.5A$ light load

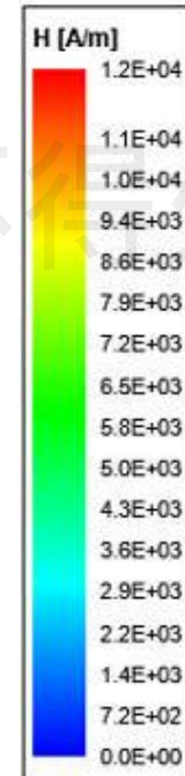

Interwinding Cap Sinking Current is Reduced Significantly by Cellular Topology


Conventional SRC

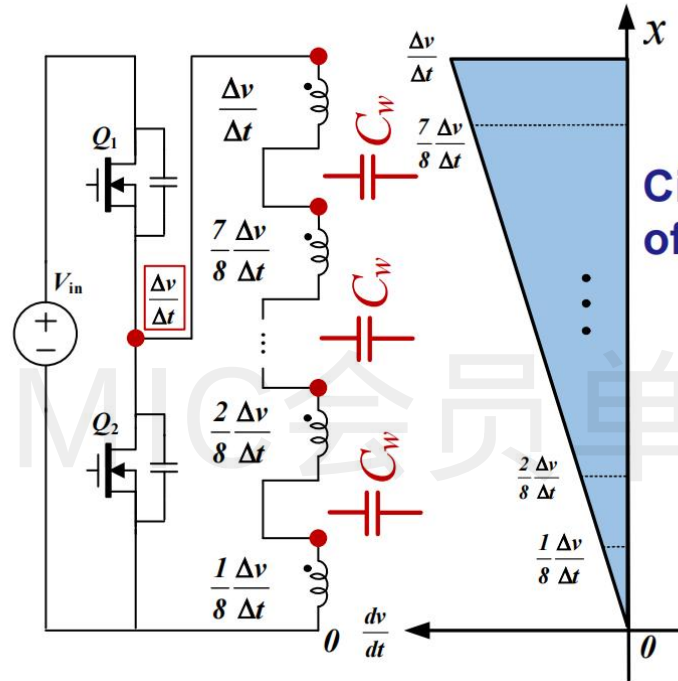

Δv : Input voltage
 Δt : Dead time

$$i_{CW} = 16C \cdot \frac{\Delta v}{\Delta t}$$

Cellular ISOP SRC

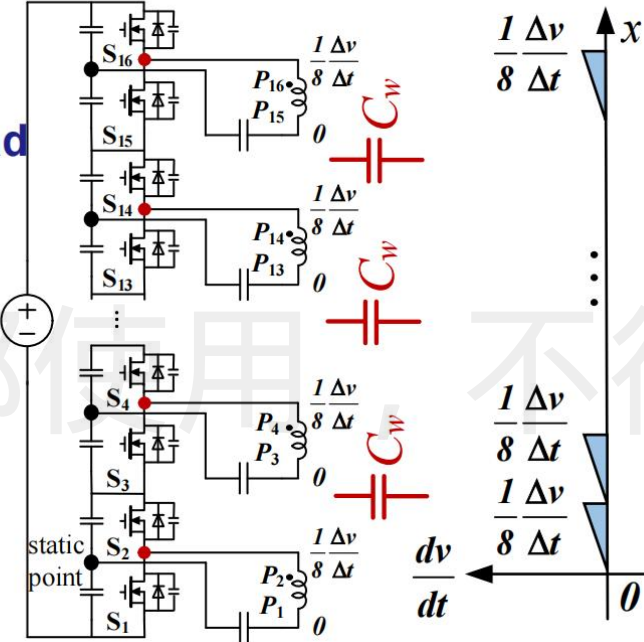


Circuit in series instead of device in series

$$i_{CW} = C \cdot \frac{\Delta v}{\Delta t}$$

Smaller magnetizing current sinking by smaller ΔV


Smaller magnetizing current and smaller eddy current loss in cellular DCX

Conventional HV SRC

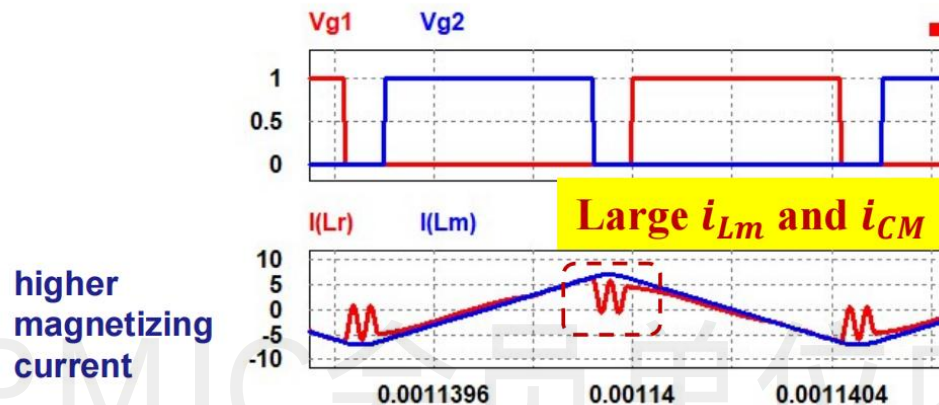


H field distribution 380V/12V DCX



@ $I_o=0.5A$

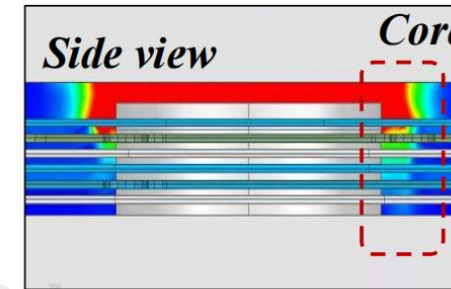

Total Winding loss $\approx 5.4W$

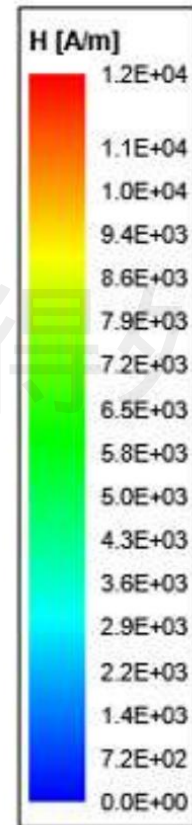

Cellular ISOP SRC

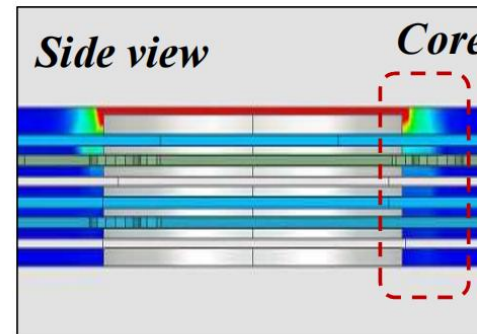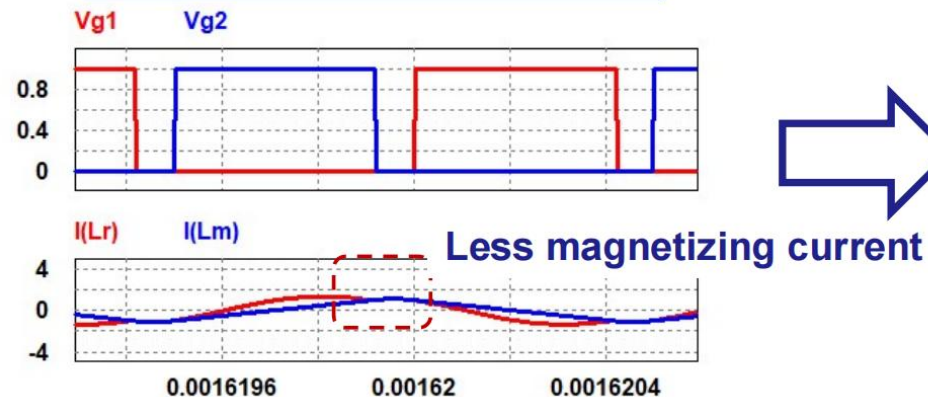


Total Winding loss $\approx 0.3W$

1st Generation 380V/12V Cellular DCX Using Low Voltage Devices






Power Management Innovation Consortium


■ Circuit cell: SRC DCX

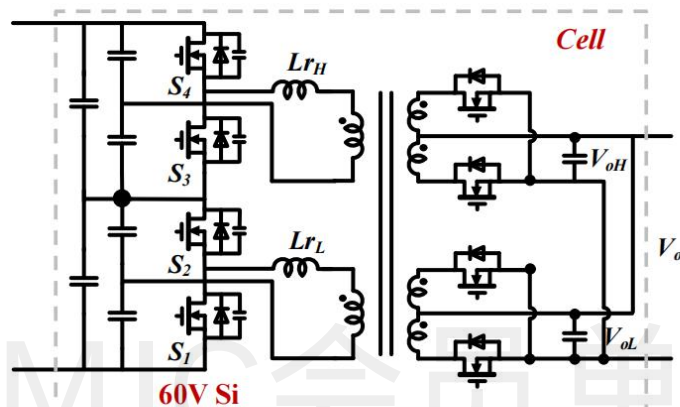


■ ISOP SRC DCX

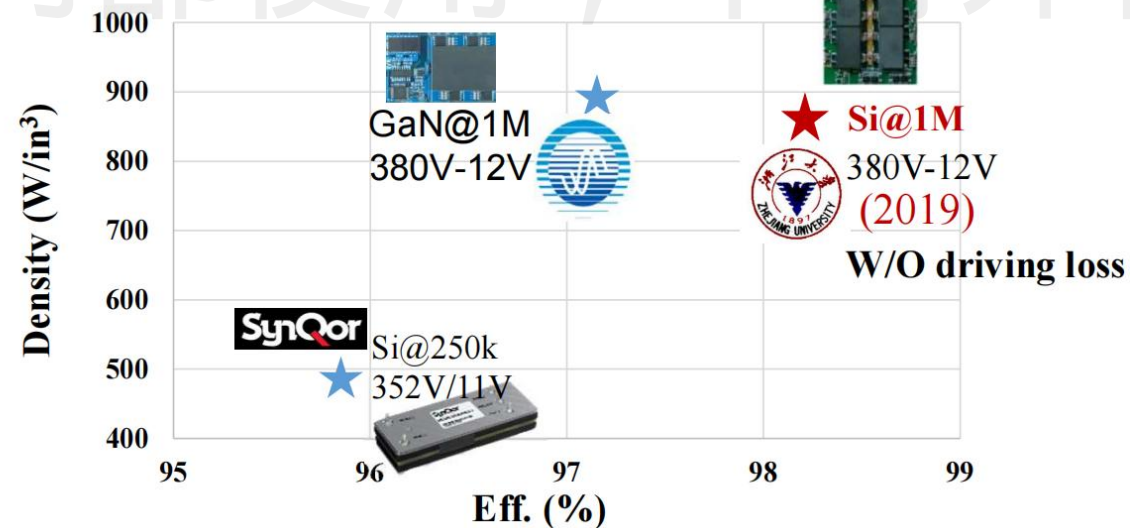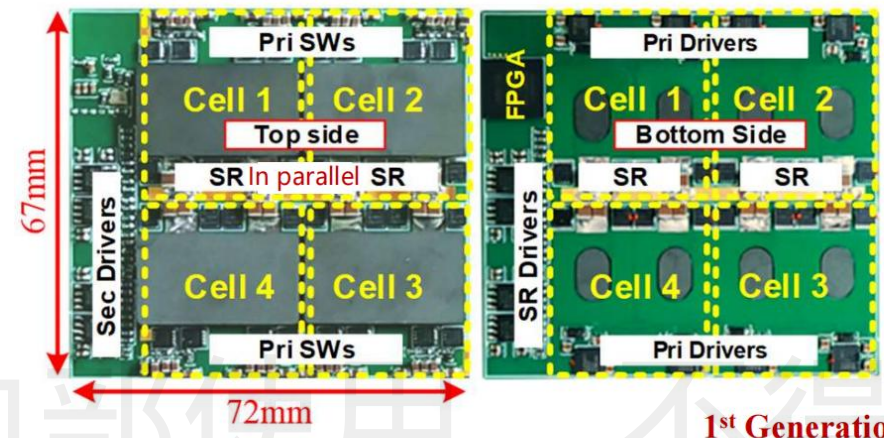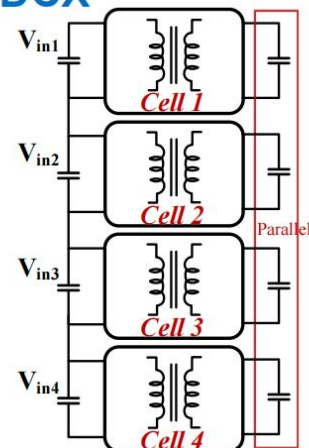

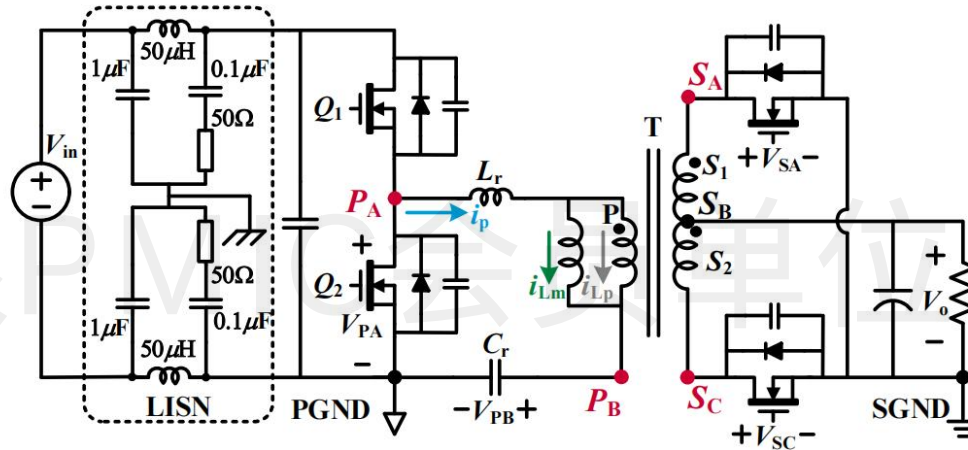CM Noise Conducting Path of the Half-bridge SRC DCX



Half-bridge SRC DCX topology with LISN

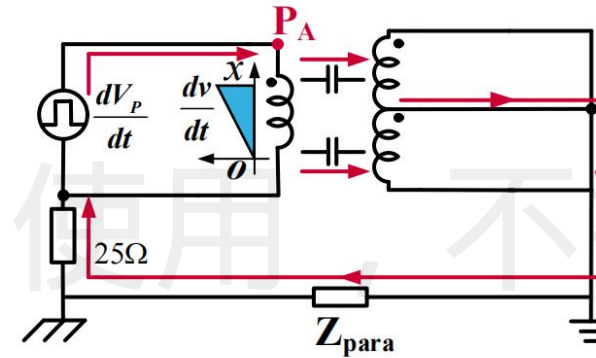


primary common mode noise source and path

[2] Yue Han, Guangcan Li, Hongbo Shi and Xinke Wu, "Analysis and Suppression of Common-Mode EMI Noise in 1 MHz 380 V-12 V DCX Converter With Low NFoM Devices," in IEEE TPEL, vol. 36, no. 7, pp. 7903-7913, July 2021.





Cellular SRC with Static Points for Smaller CM Current and Noise

Conventional HV SRC


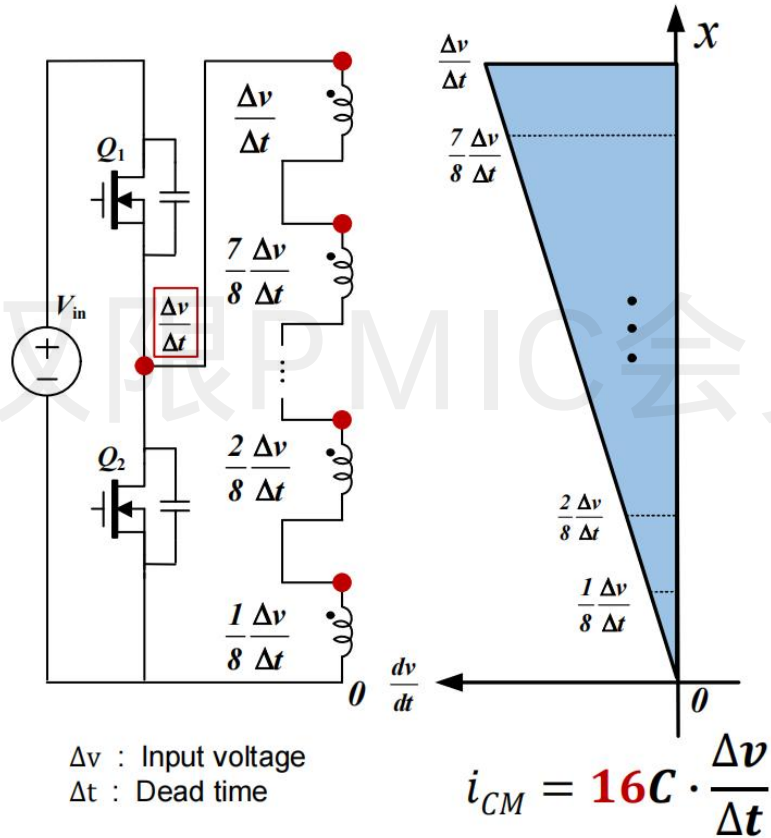


ISOP Cellular SRC

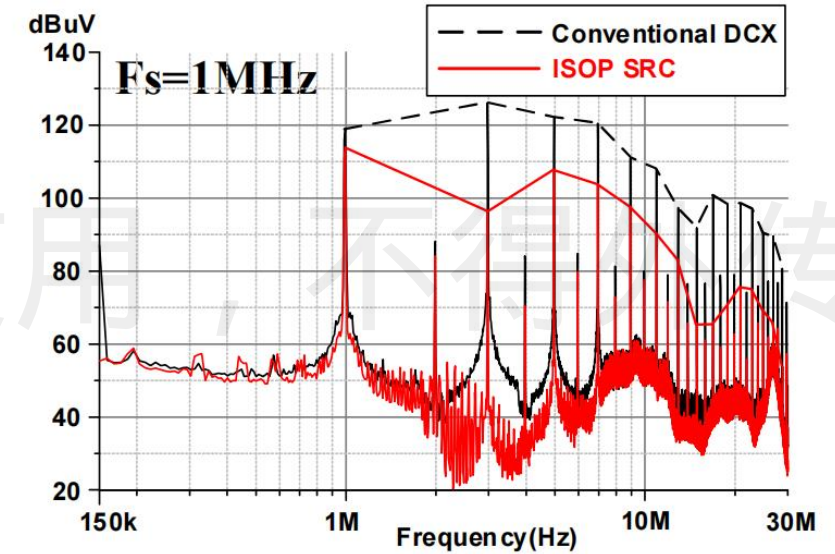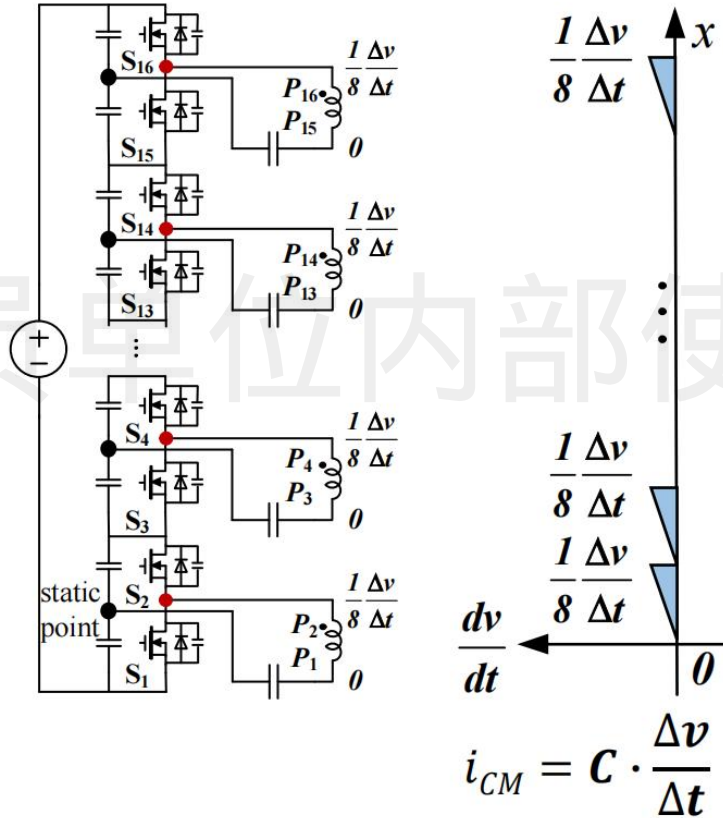

Common-mode Noise Cancellation with Inversing Driving Logic in the Cellular DCX

■ Inverse driving in ISOP SRC

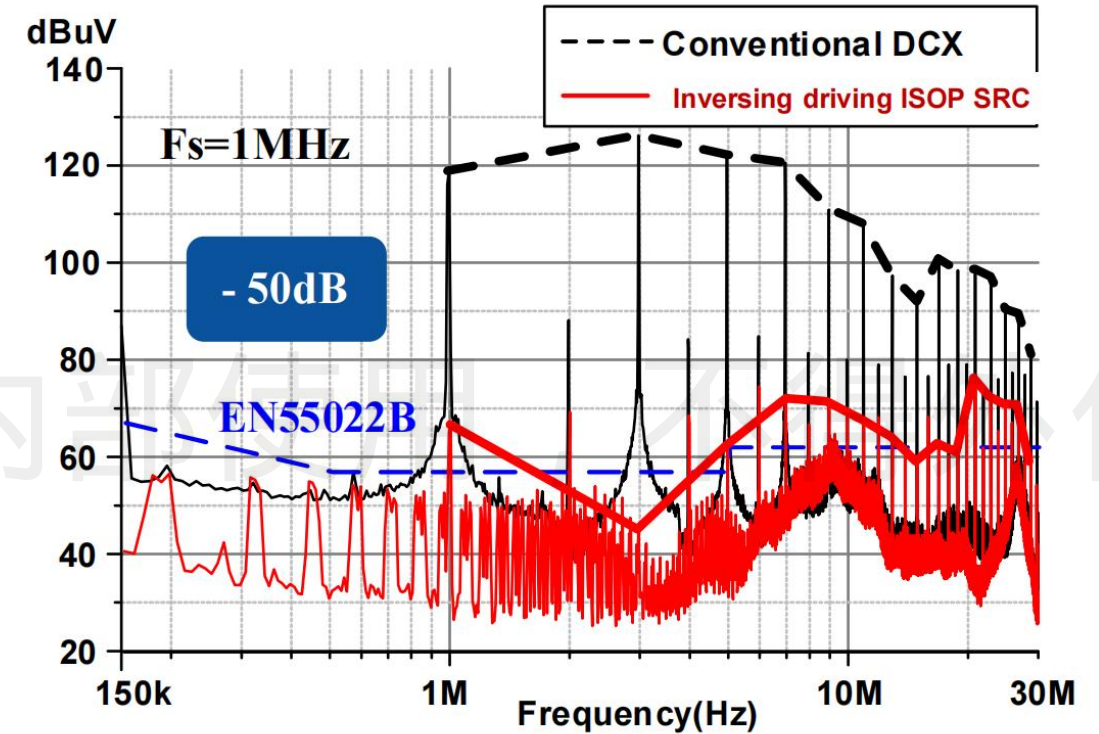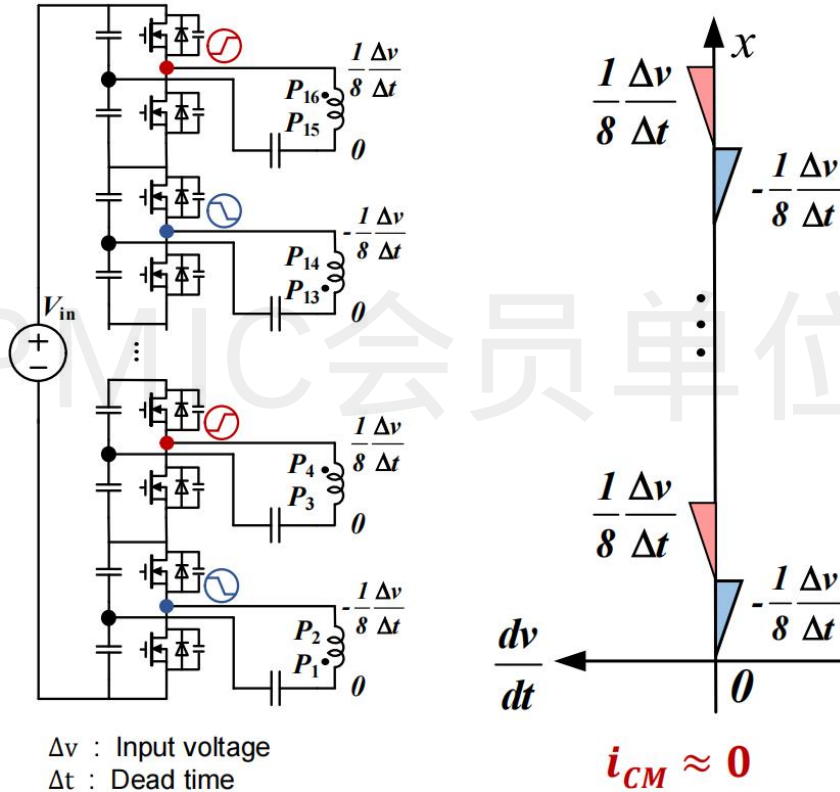


No need for shielding layers

[2] Yue Han, Guangcan Li, Hongbo Shi and Xinke Wu, "Analysis and Suppression of Common-Mode EMI Noise in 1 MHz 380 V-12 V DCX Converter With Low NFoM Devices," in IEEE TPEL, vol. 36, no. 7, pp. 7903-7913, July 2021.





Large Driving Loss when Using Drive ICs

□ 1MHz 380V-12V-150A DCX

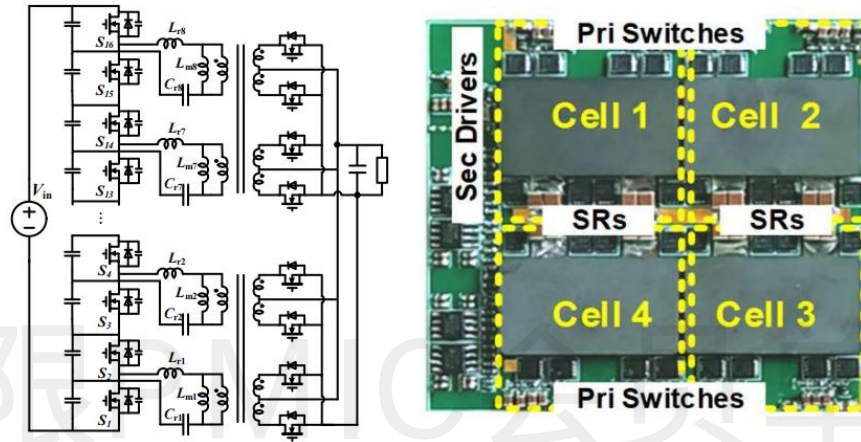

	Primary MOSFET	Synchronous Rectifier
Type		
	BSZ040N06LS5	BSZ0501NSI
Quantity	16	32
Q_g (nC@7V)	25.7	17.5

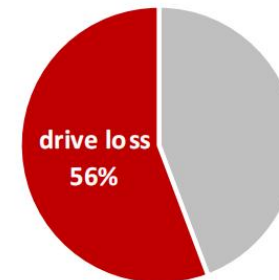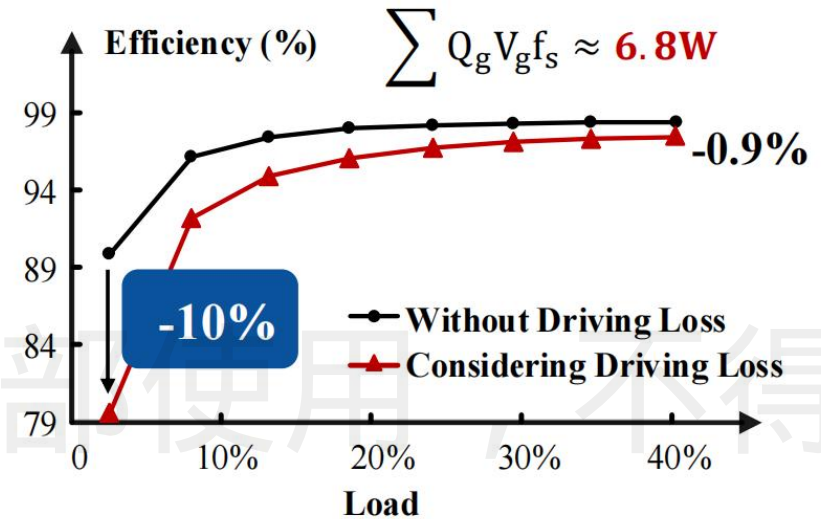


Light load
3% of full load



Light load efficiency
reduced significantly


Lower Driving Speed Results in Less Driving Loss in Resonant Driver

➤ Voltage source driver (VSD)

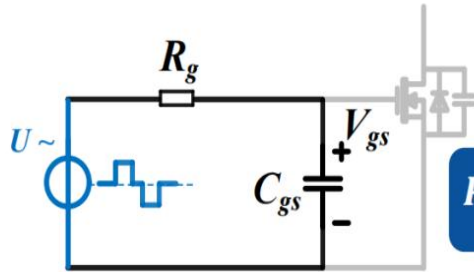


$$P_{dri} = C_{gs} V_{gs}^2 f_s$$

➤ Resonant driver

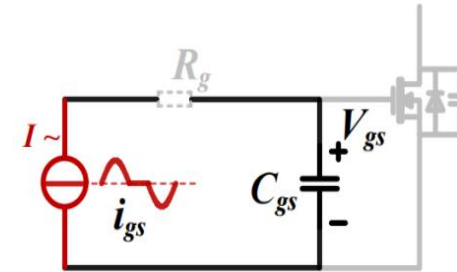


Ideal
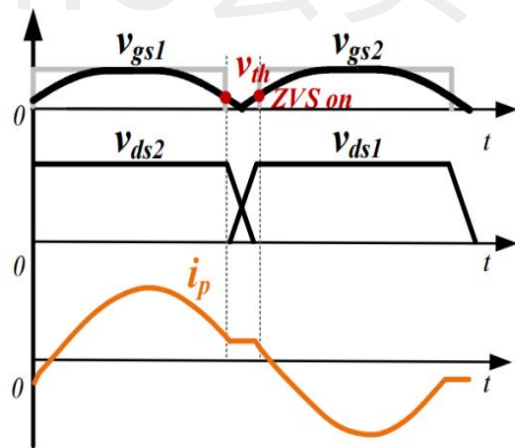
$$P'_{dri} = i_{gs}^2 R_g \rightarrow 0$$




Primary ds voltage and current in SRC converter

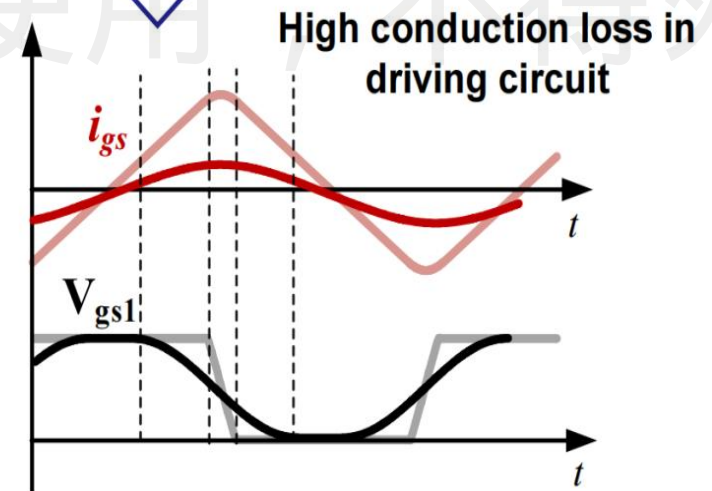Lower driving speed is acceptable owing to sinusoidal switch current





Less driving current is needed

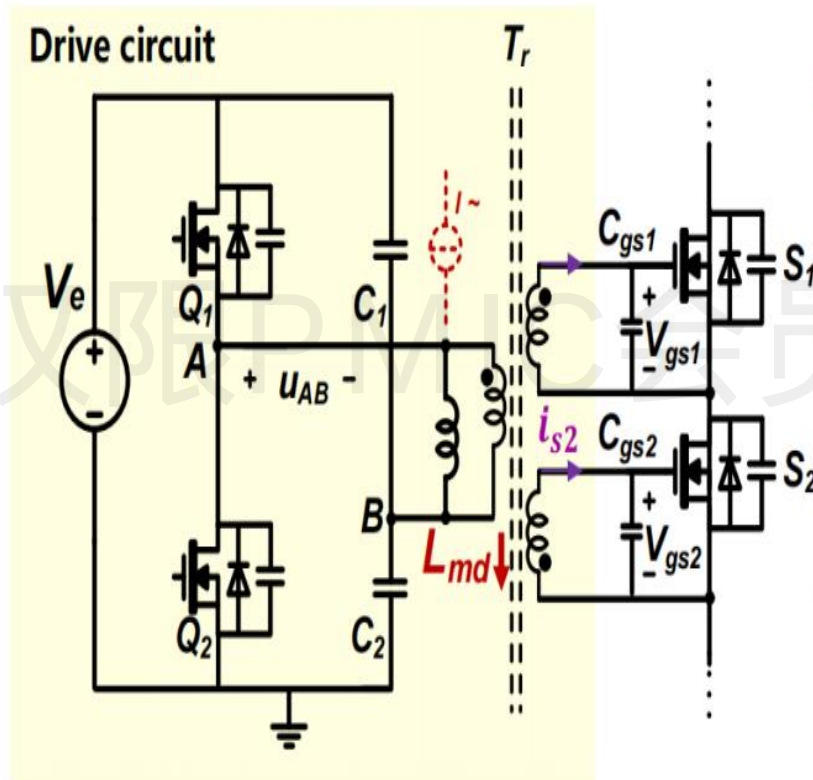Driving Loss Reduced Significantly By the Resonant Drive Transformer



ZVS for driving circuit

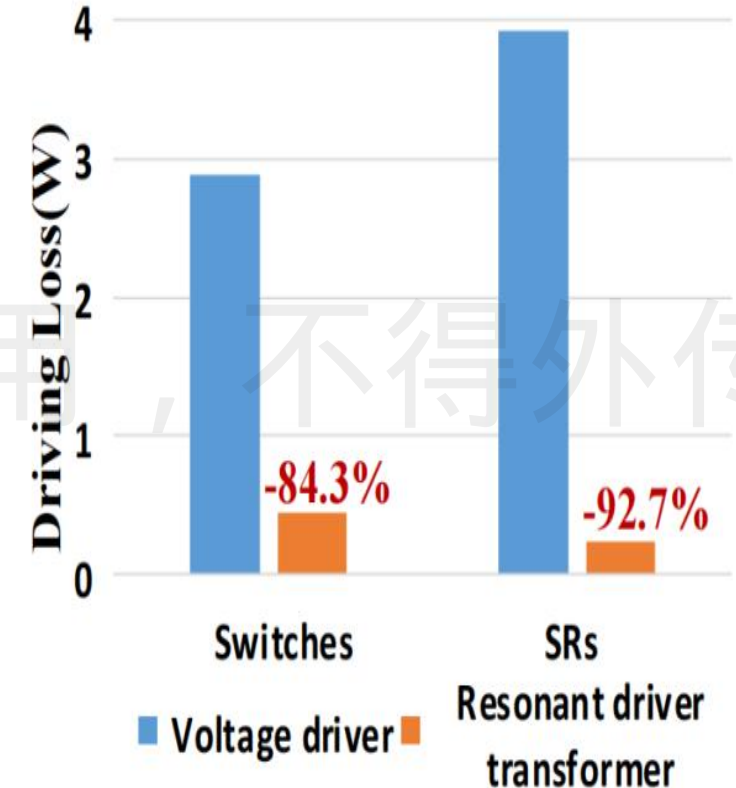
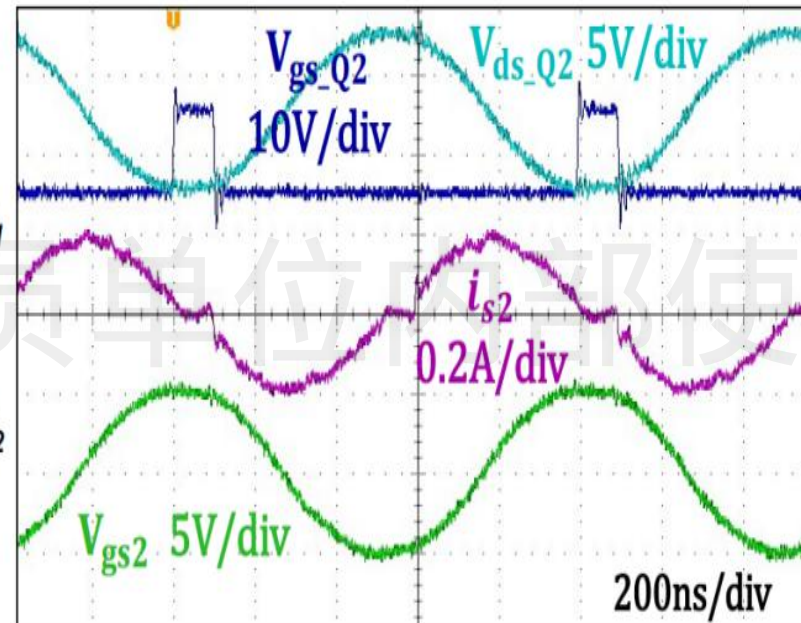


Resonant Drive Transformer


- ✓ Save driving losses
- ✓ Shrink the footprint of drive circuit

Integrating More PCB Layers for Power Density Optimization

➤ 1st Generation

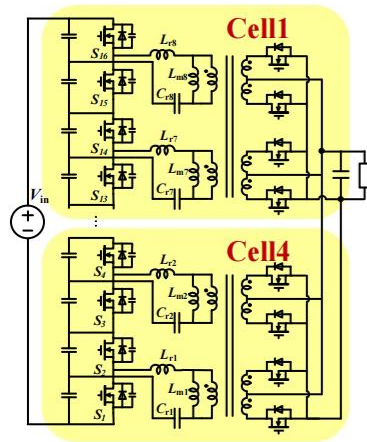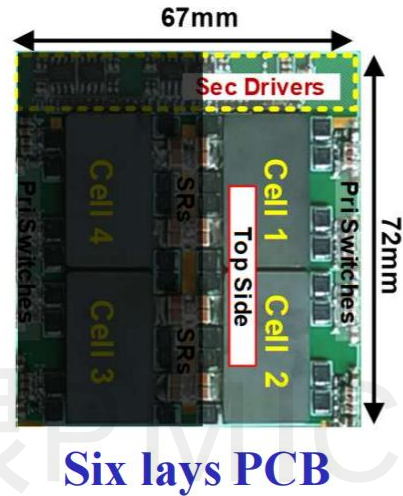


■ Transformer =4

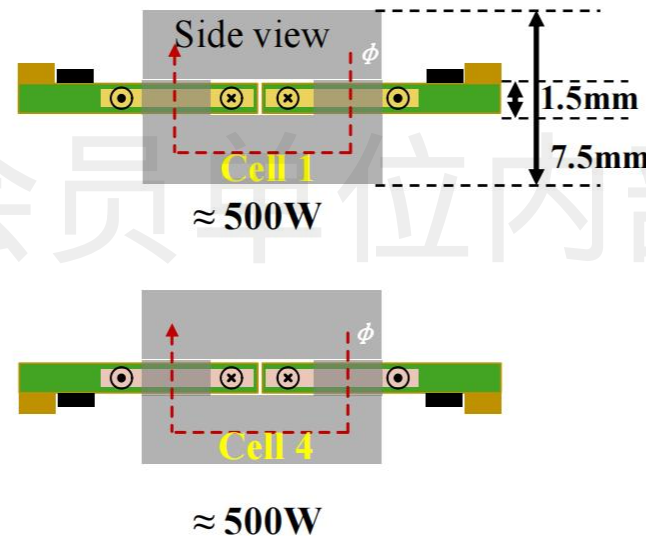

■ Transformer =2


12 lays PCB

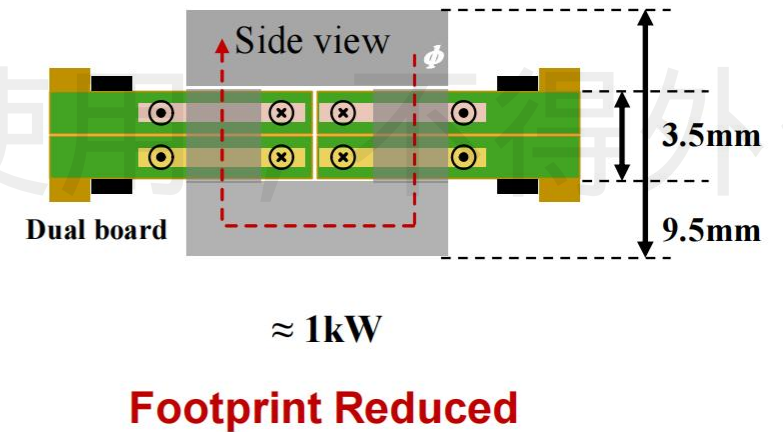

Cellular topology makes higher integrated transformer easier

2nd Generation 380V/12V DCX Using Resonant Drive Transformer and Integrated Power Transformer


■ Comparison of the prototypes

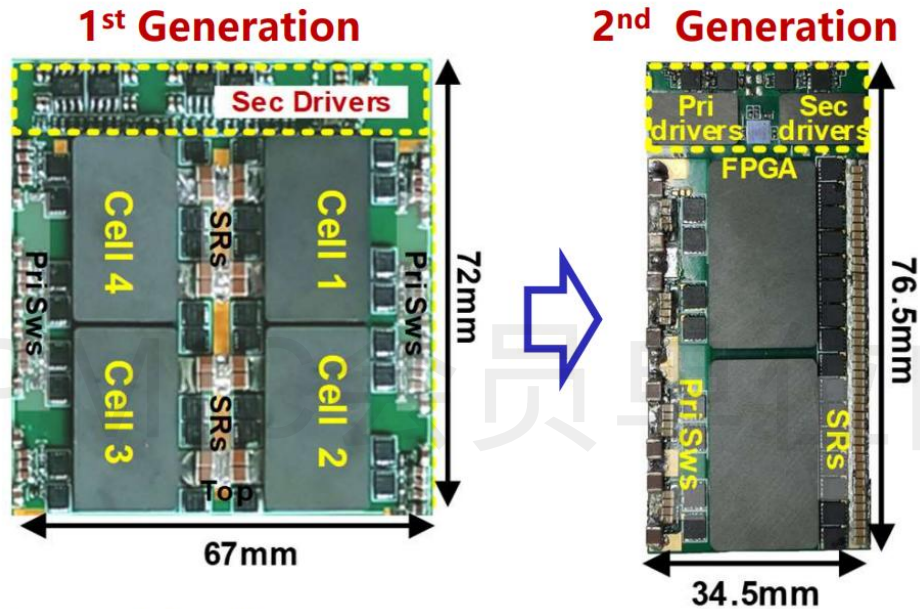

■ Power Density:

~0.9kW/in³

~1.3kW/in³

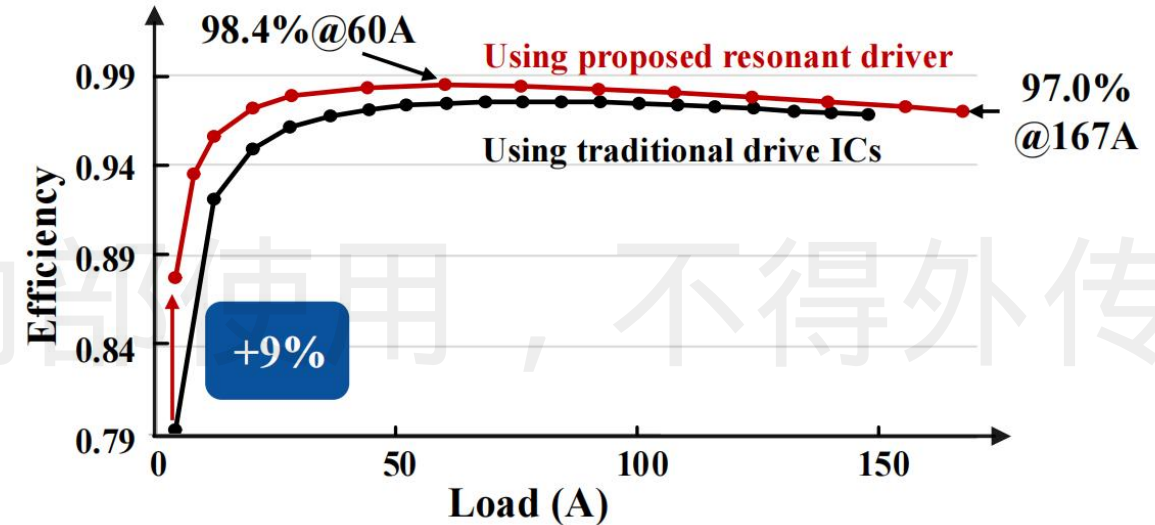



Considering the driving losses

[3] Guangcan Li and Xinke Wu, "A 98.4% Efficiency 380V-12V DCX With 1.3kW/in³ Power Density Using Low NFoM Devices and Resonant Drive Transformer," in IEEE TPEL, vol. 37, no. 10, pp. 12346-12356, Oct. 2022.




Less Power Density Improvement when Further Reducing the Thickness of Plate Core

Core plate is thicker than chips



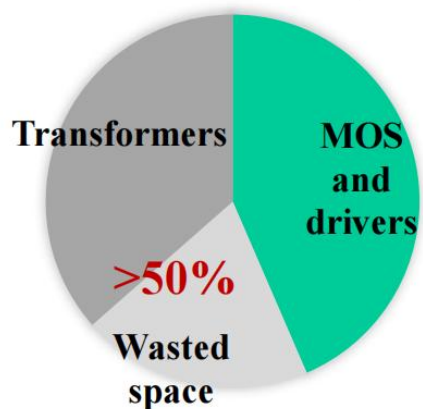
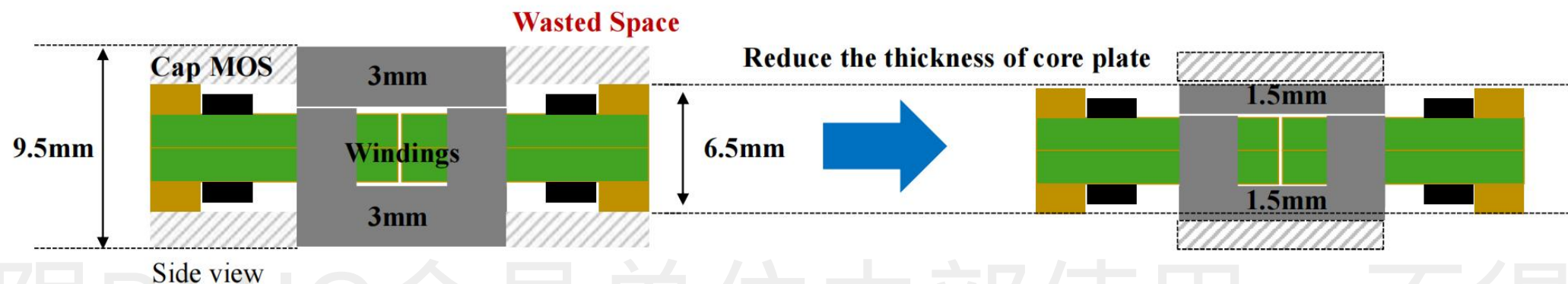


■ Volume Breakdown

■ Loss Breakdown @ peak efficiency



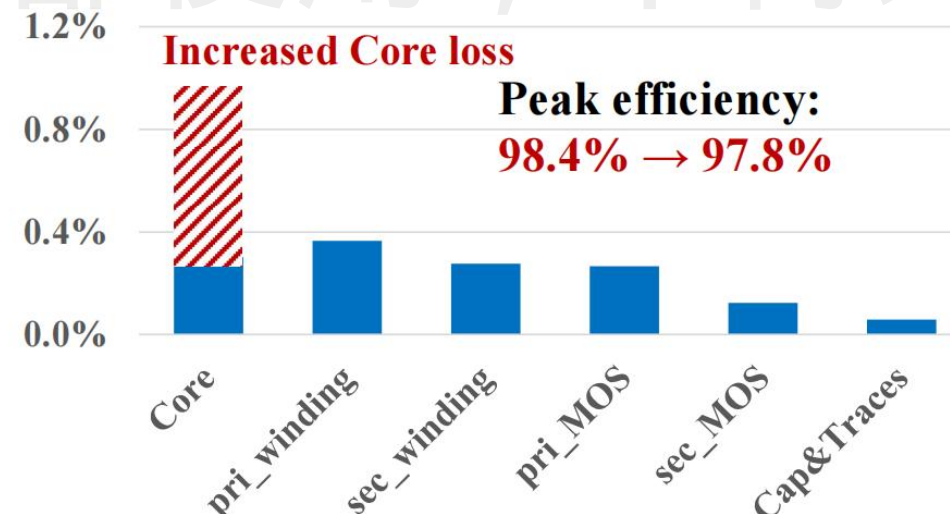


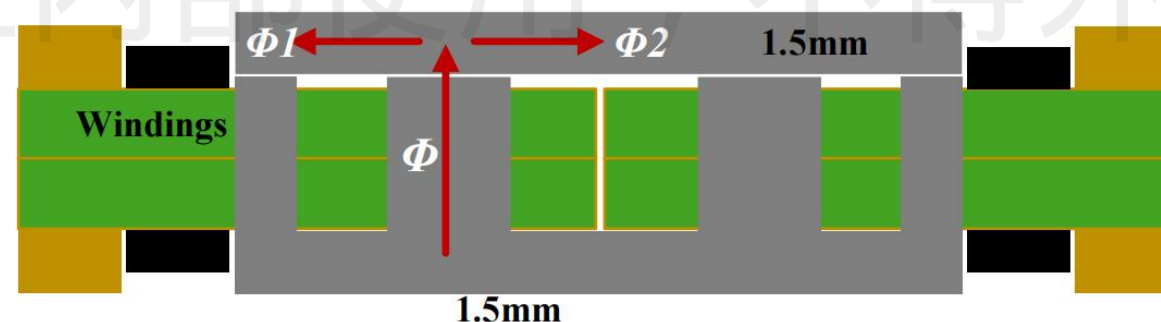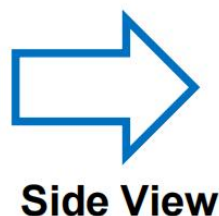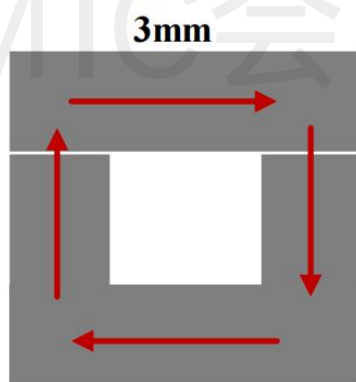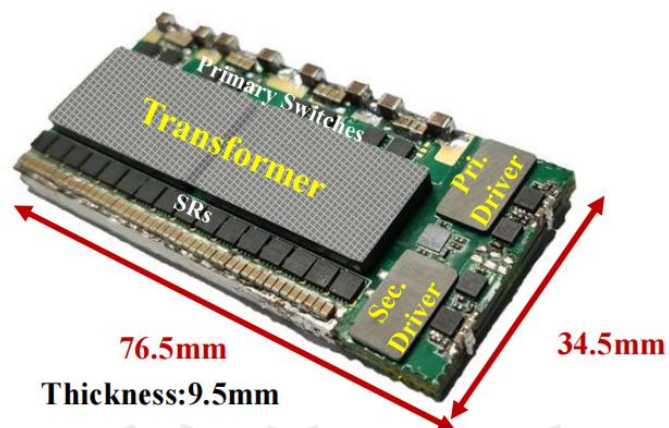Multi-window EI Core for Shrinking Plate Thickness




- Large thickness resulted by single-side flux flow in U Core

How to guarantee $\Phi 1 = \Phi 2$?

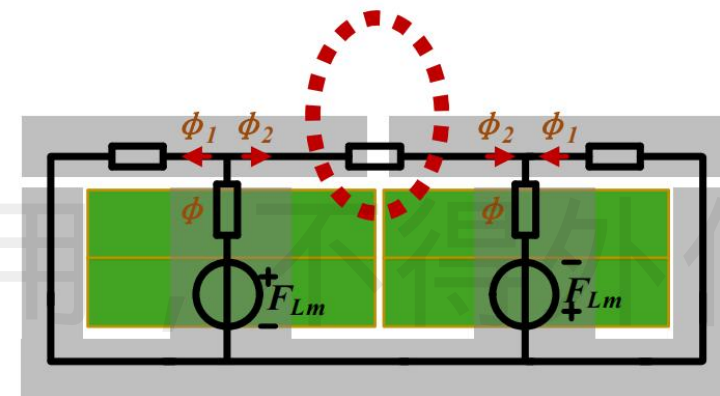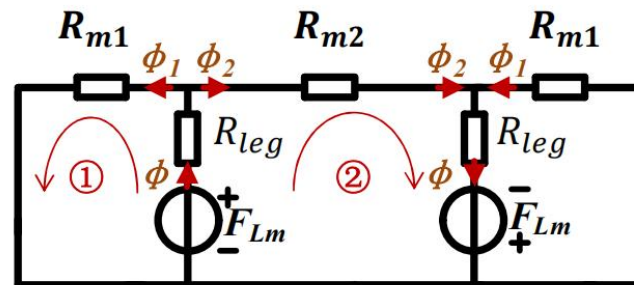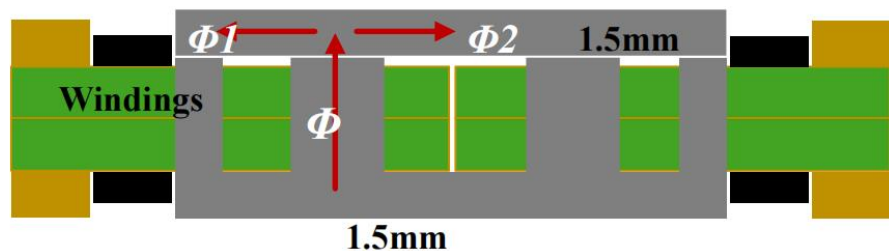

Magnetic resistance model

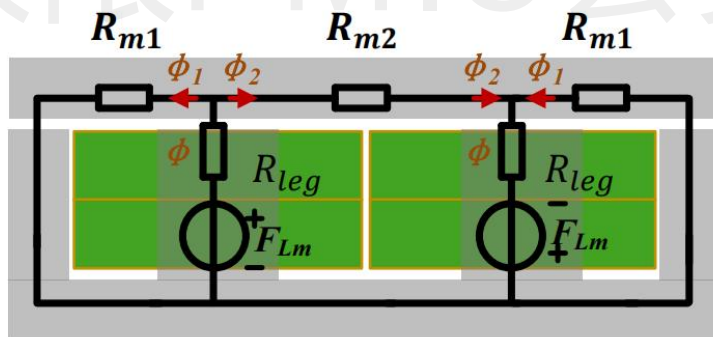



$$\begin{aligned} \textcircled{1} \quad F_{Lm} - \Phi R_{leg} &= \Phi_1 R_{m1} \\ \textcircled{2} \quad 2F_{Lm} - 2\Phi R_{leg} &= \Phi_2 R_{m2} \\ \textcircled{1} \times 2 \quad 2F_{Lm} - 2\Phi R_{leg} &= 2\Phi_1 R_{m1} \end{aligned}$$

$$\frac{\Phi_1}{\Phi_2} = \frac{R_{m2}}{2R_{m1}}$$


$$R_{m2} = 2R_{m1} \text{ to make } \Phi_1 = \Phi_2$$

Comparison Between the Prototype Using U Cores (2G) and Multi-window EI Core (3G)

➤ Efficiency of the Prototype

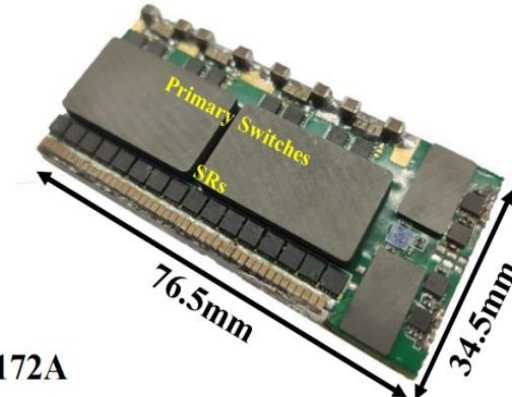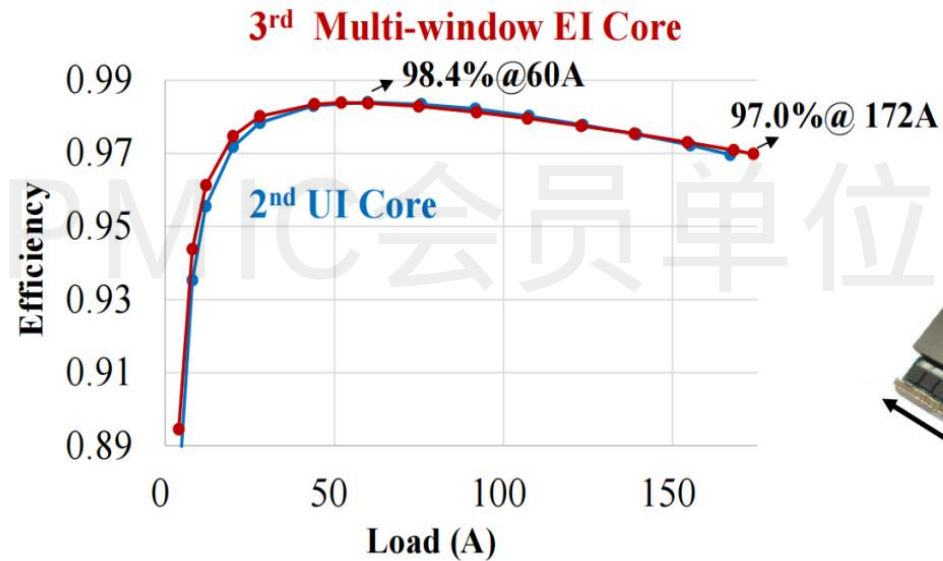

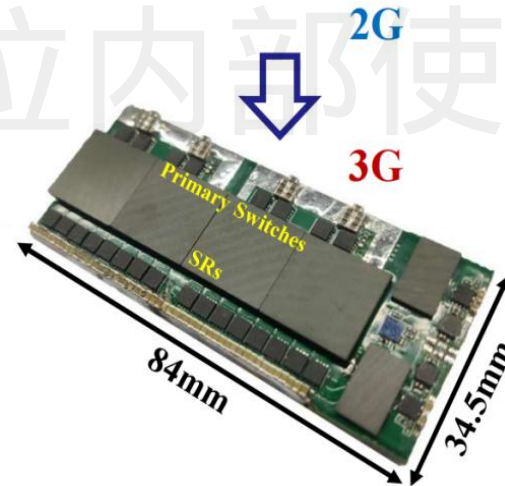
Peak efficiency: 98.4%
density: **1300W/in³**




Input: 380Vdc
Output: 12Vdc – 172A
Frequency: 1MHz
Peak efficiency: 98.4%
Density: **1800W/in³**

[4] Guangcan Li and Xinke Wu, "A 1.8kW/in³ Power Density Cellular 380V-12V DCX with 98.4% Peak Efficiency Using Low NFoM Devices and Resonant Drive Transformer," in PEAC 2022 (Accepted).


Loss Breakdown of the 3G Prototype

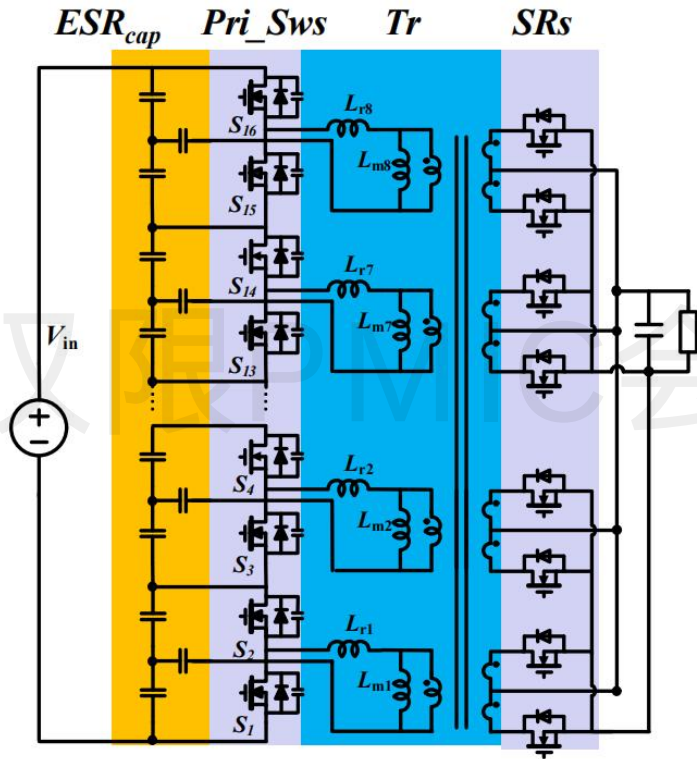

➤ Loss under different load

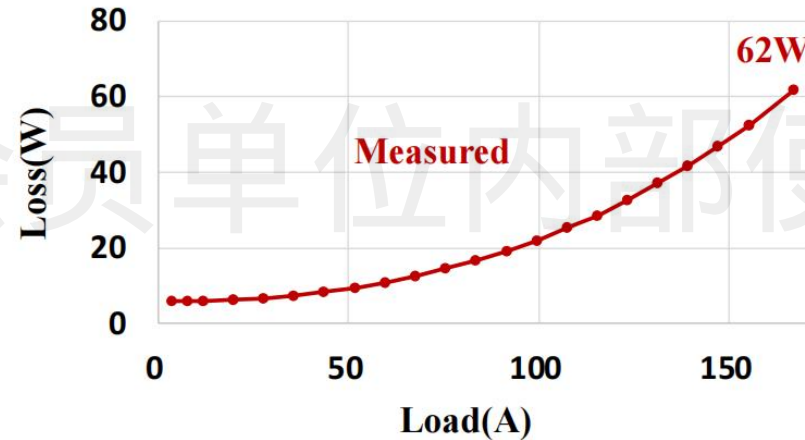


Loss Breakdown @Full Load

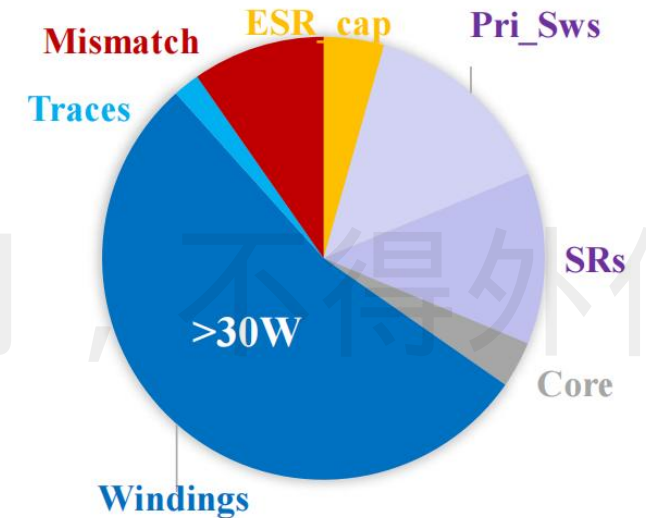





Large winding loss @full load

Eddy Current Loss of the Windings

➤ Loss Breakdown @ Full load

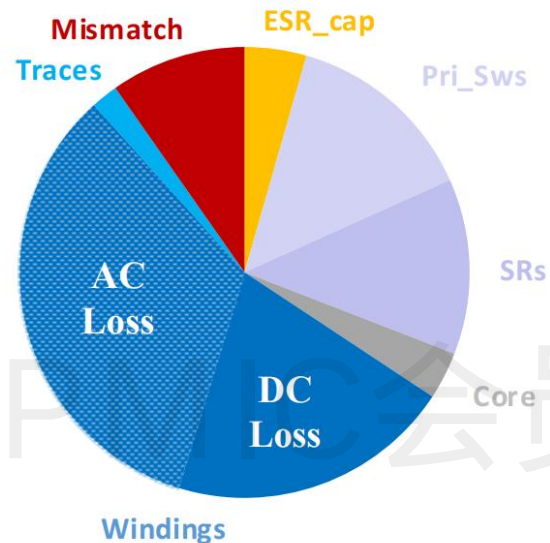


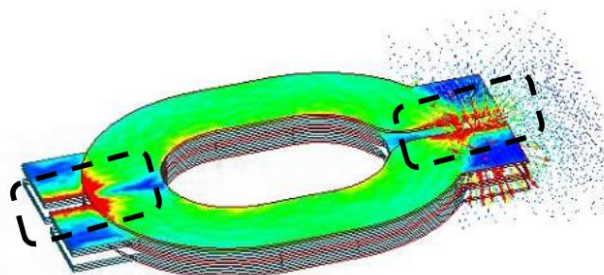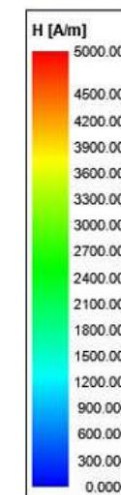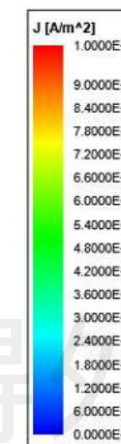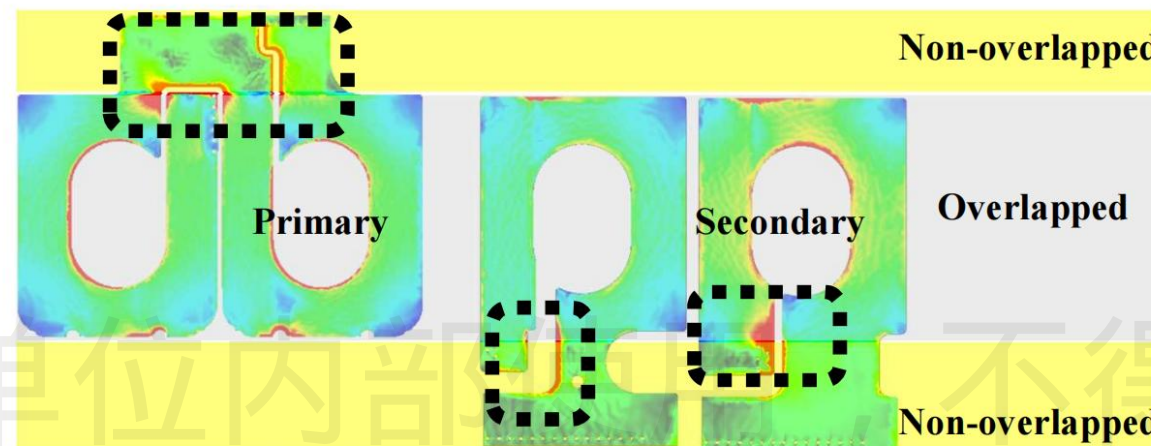■ Large termination loss on windings @ 1MHz




Typical Termination Loss Reduction Methods and 4th Generation Prototype

■ Original structure

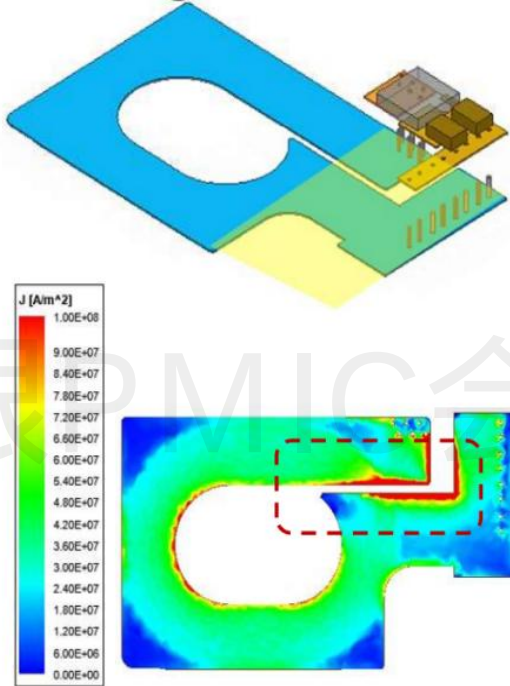


Non-overlapped Termination results in large eddy current

■ Method 1

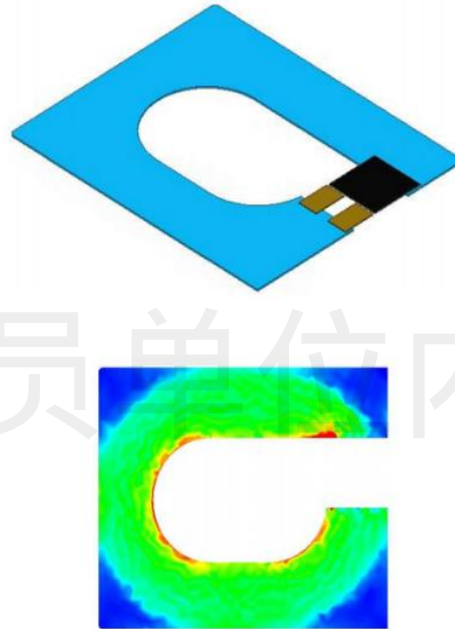


Integrate SRs on windings

■ Method 2

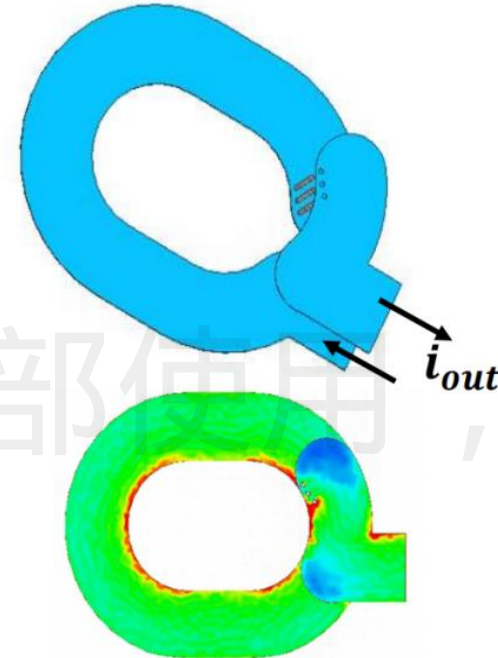

Interleave the termination

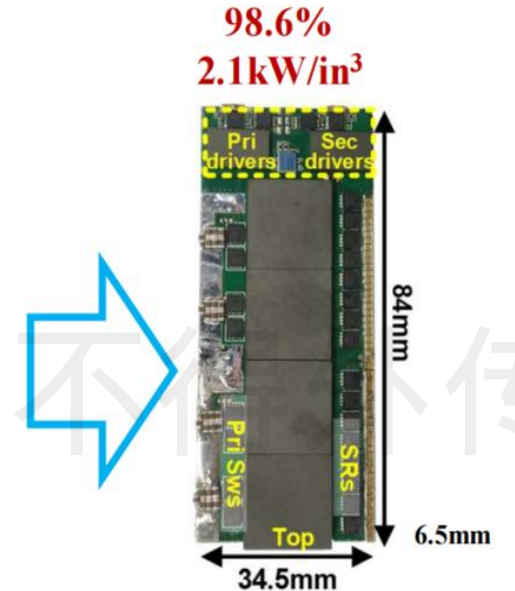


Efficiency Improvement with Termination Optimization


Input: 380Vdc

Output: 12Vdc


➤ After termination optimization

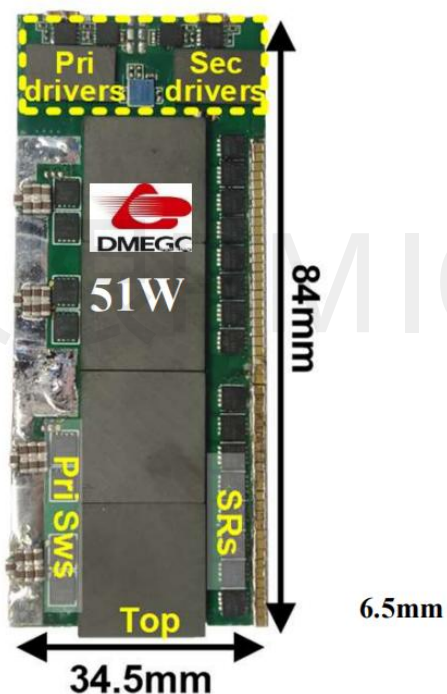

4th Generation

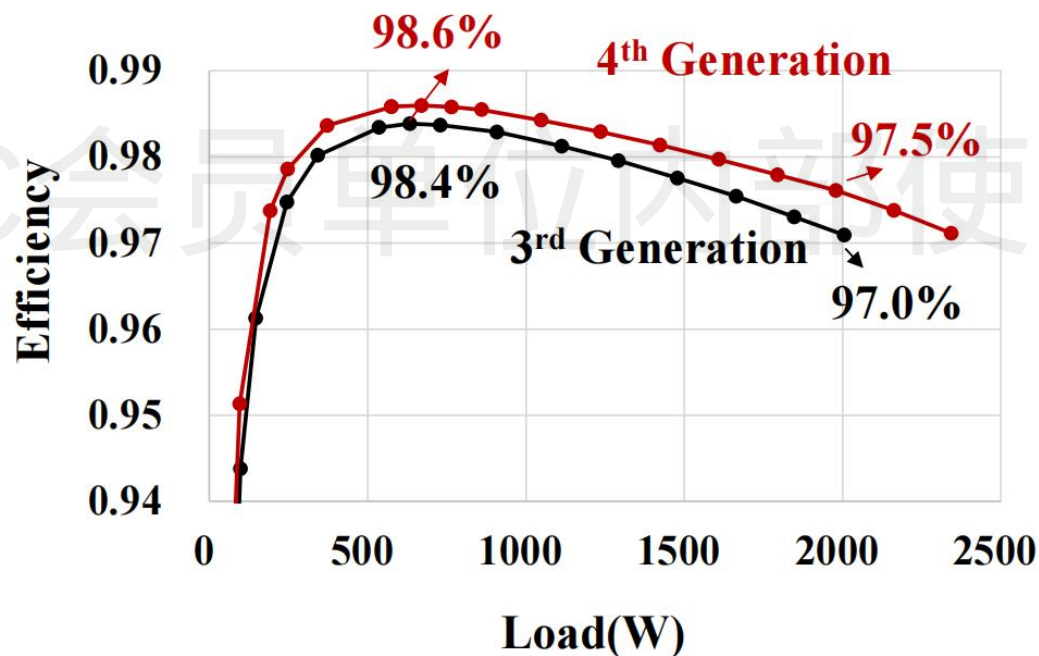


■ Loss Breakdown @ Po=2kW

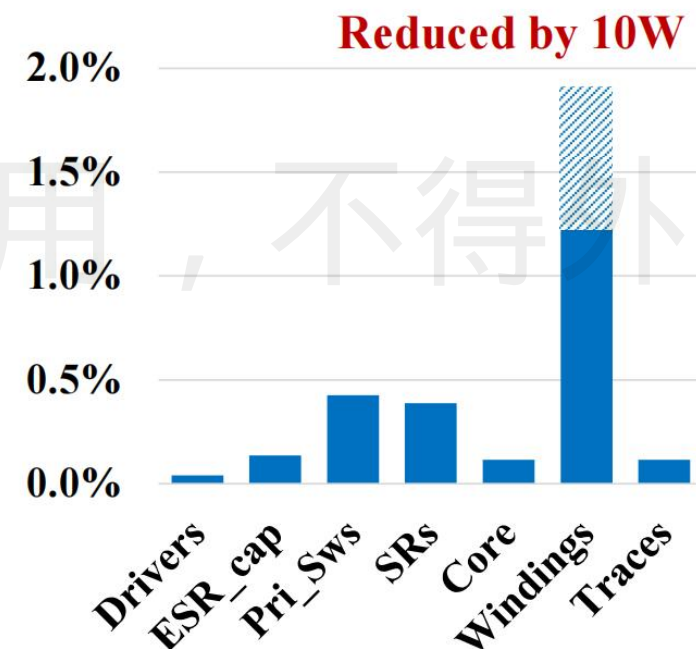

Evolution of 1MHz 380V/12V 2kW Prototypes

Peak Efficiency
Power Density


97.3%
0.8kW/in³

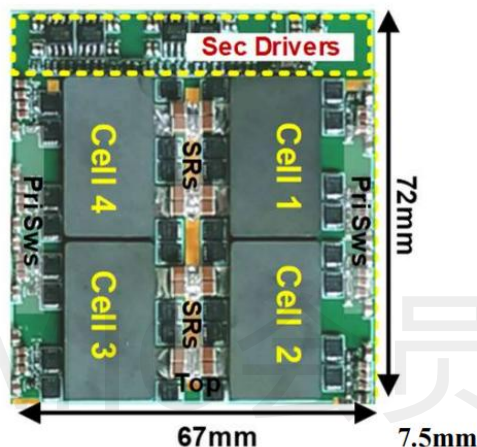

(2018)

Resonant Drive Tr.


98.4%
1.3kW/in³

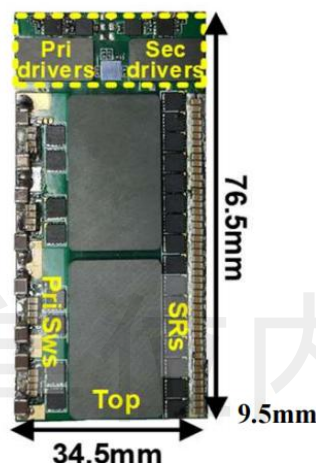

(2020)

Multi-window EI Tr.


98.4%
1.8kW/in³

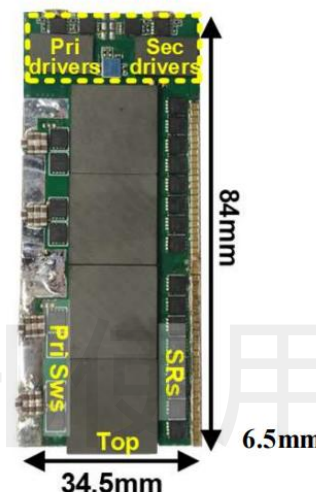

(2022. May)

Termination optimizing

98.6%
2.1kW/in³

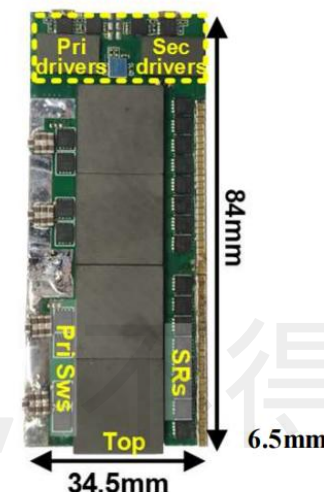

(2022. Nov.)


1st G

2nd G

3rd G

4th G

380V-12V DC/DC模块技术发展

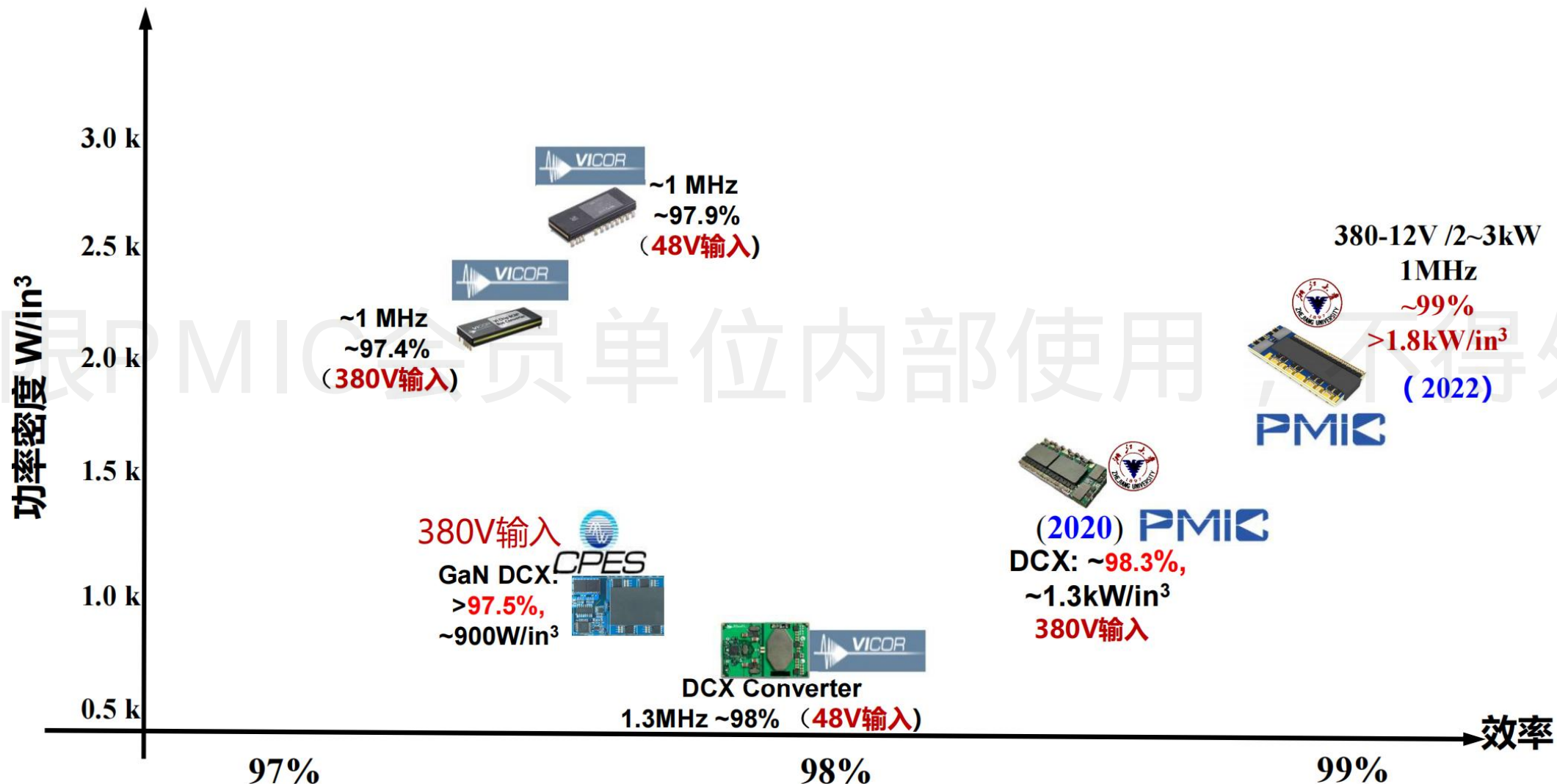

感谢电源管理技术创新联盟(PMIC)资助!

PMIC

Power Management Innovation Consortium





高校主导、行业共建的电源管理技术生态链

器件

装置

系统

矽力杰半导体

杰华特半导体

派恩杰电子

纳微半导体

英诺赛科

横店东磁

希磁科技

必易微电子

晶丰明源

深圳英飞源技术

杰瑞电子(716所)

长城电源

杭州英飞特新能源

铂科电子

奥海科技

昕诺飞(原飞利浦)

酷科电子(紫米)

杭州富特科技

麦田能源

OPPO技术

台达电子

VIVO技术

汇川技术

中兴通讯

安克创新

国内首个

合作生态

模式探索

未来技术






仅限PMIC会员单位内部使用 不得外传

Thanks for your time



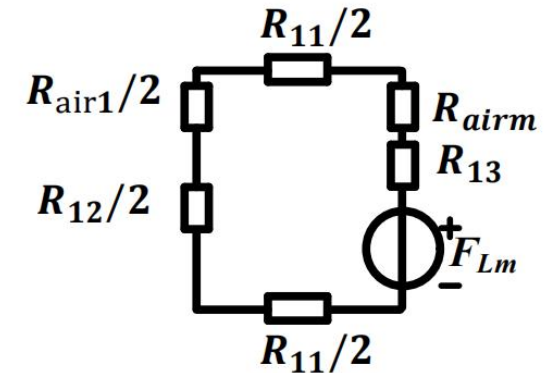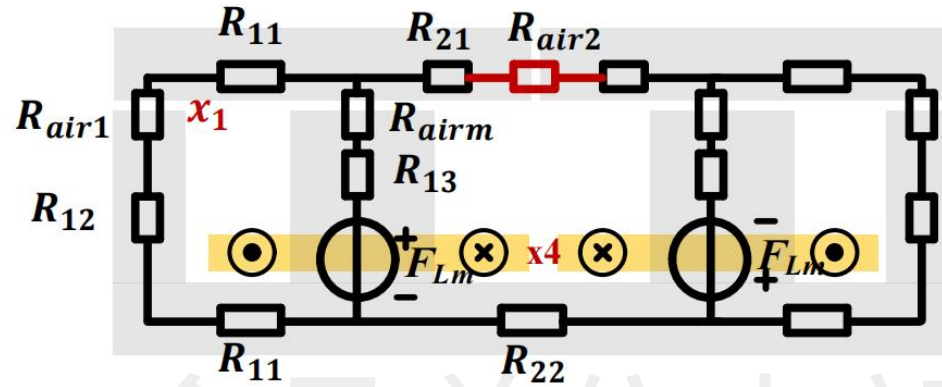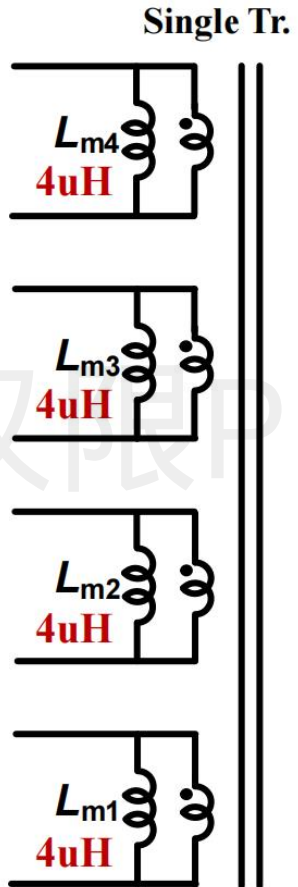Backup - Appendix A — Calculation of the Airgap




Equivalent Loop for L_m calculation


$$\left\{ \begin{array}{l} R_{air1} = \frac{x_1}{0.5\mu_0 A e} \\ R_{airm} = \frac{x_1}{\mu_0 A e} \\ 16\mu H \approx 2 * 4^2 * \frac{1}{R_{airm} + R_{air1}/2} \\ \sum R_{2i} + R_{air2} = 2(\sum R_{1i} + R_{air1}) \end{array} \right.$$


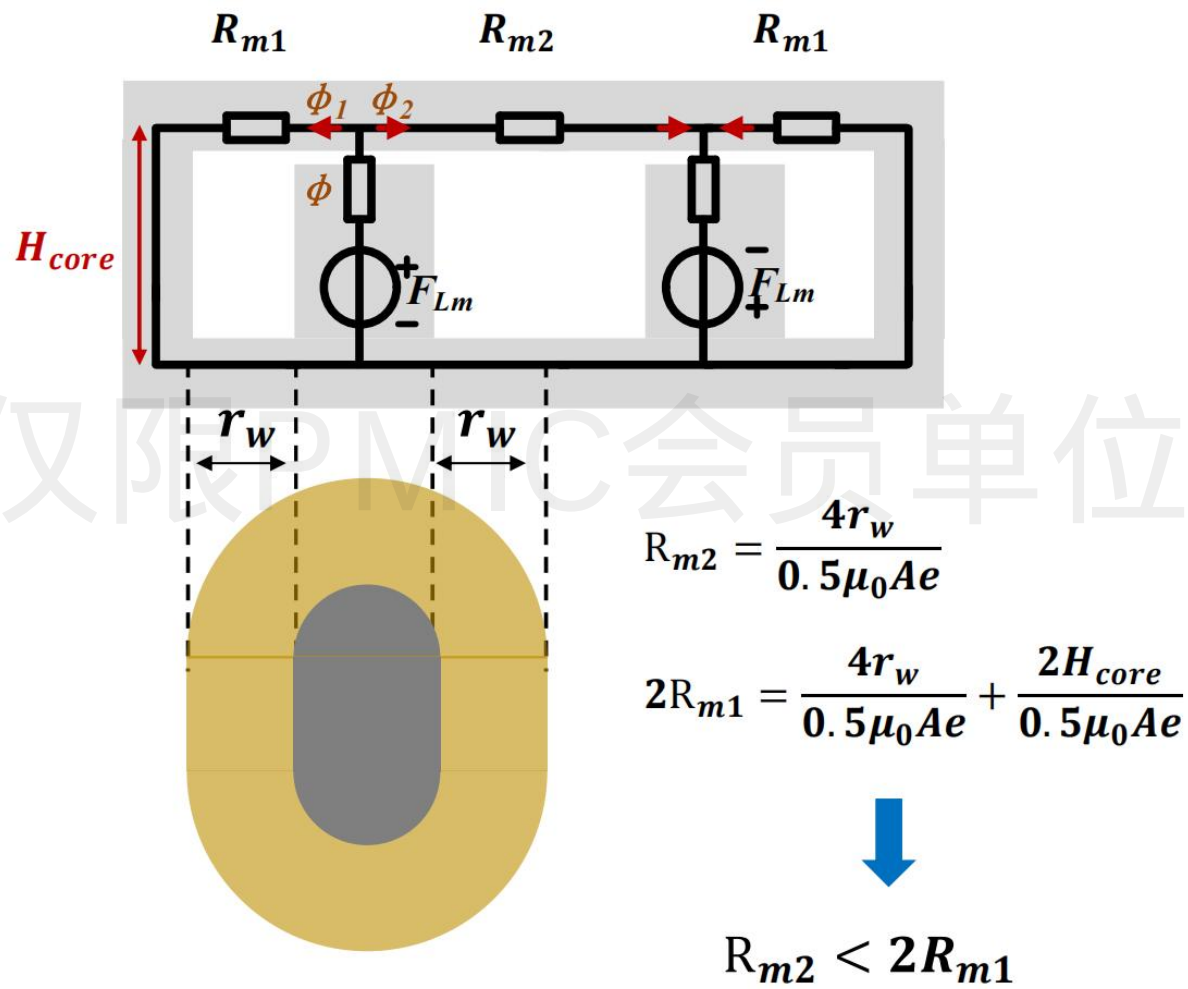
$$x_1 \approx 60\mu m, x_2 \approx 130\mu m$$



3D Simulation Results

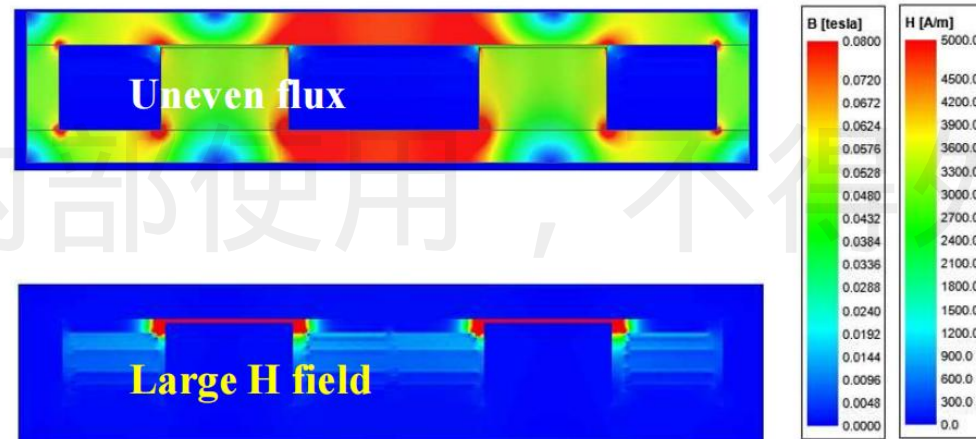



Total winding loss $\sim 0.5W$ @0.4A I_o

Larger t_d Leads to Less Pri. Conduction Loss




Normalized primary conduction loss:

η : efficiency
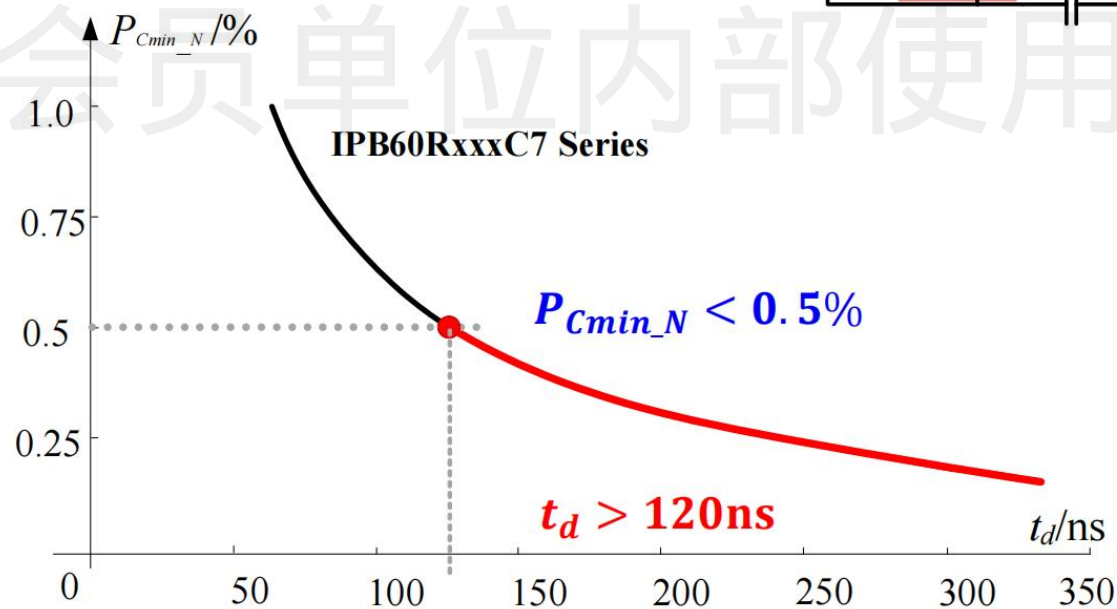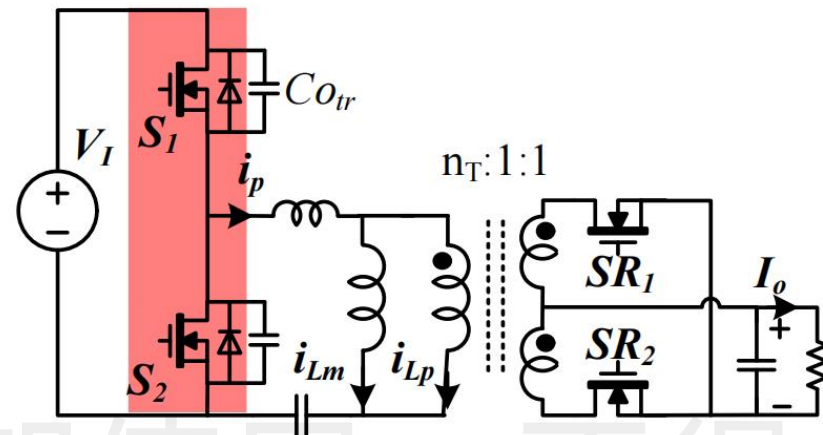
$$P_{Cmin_N} = \frac{P_{Cmin}}{P_o} = \frac{2\pi\eta * NFoM}{t_d}$$




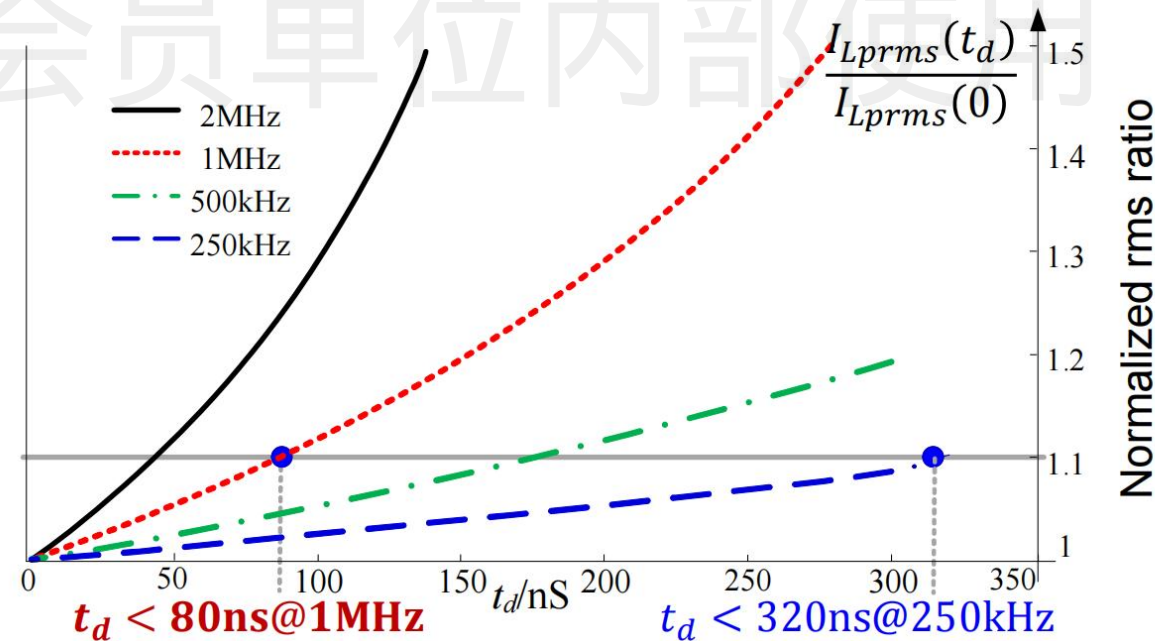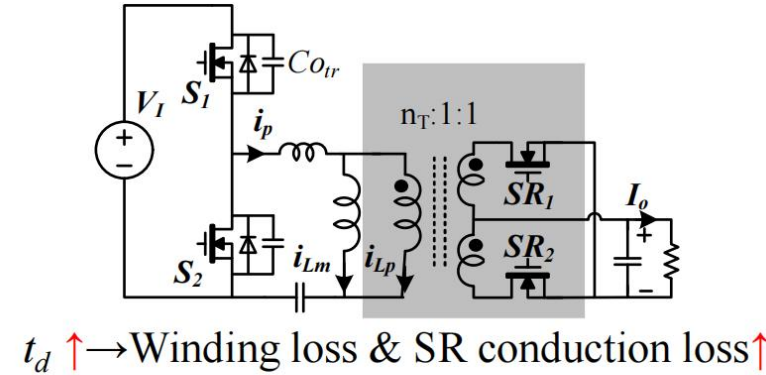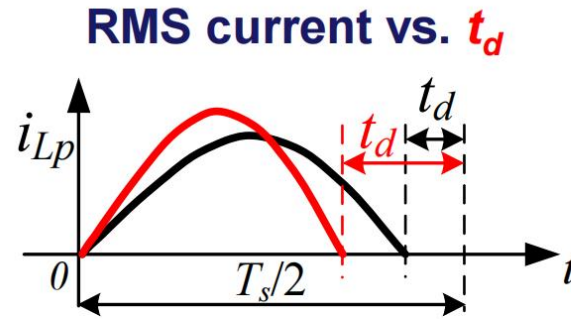Larger t_d Results in higher RMS Current in Windings



Great Challenge between Pris. and Winding Loss at MHz Level Achieving High Efficiency
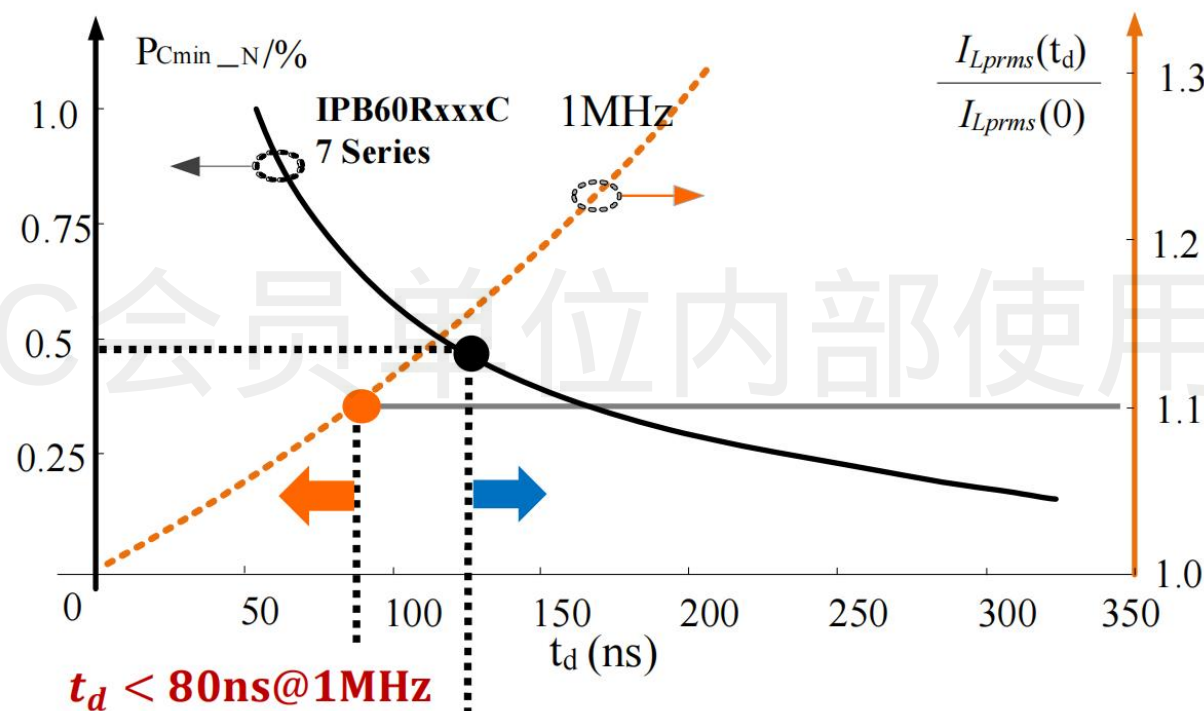
$$P_{Cmin_Normalized} = \frac{2\pi * \eta * NFoM}{t_d}$$




No Overlap @ 1M

Impossible of 98% efficiency with Current High Voltage Si devices.



Achieve High Efficiency at MHz when Using Series Connected Low NFoM Devices
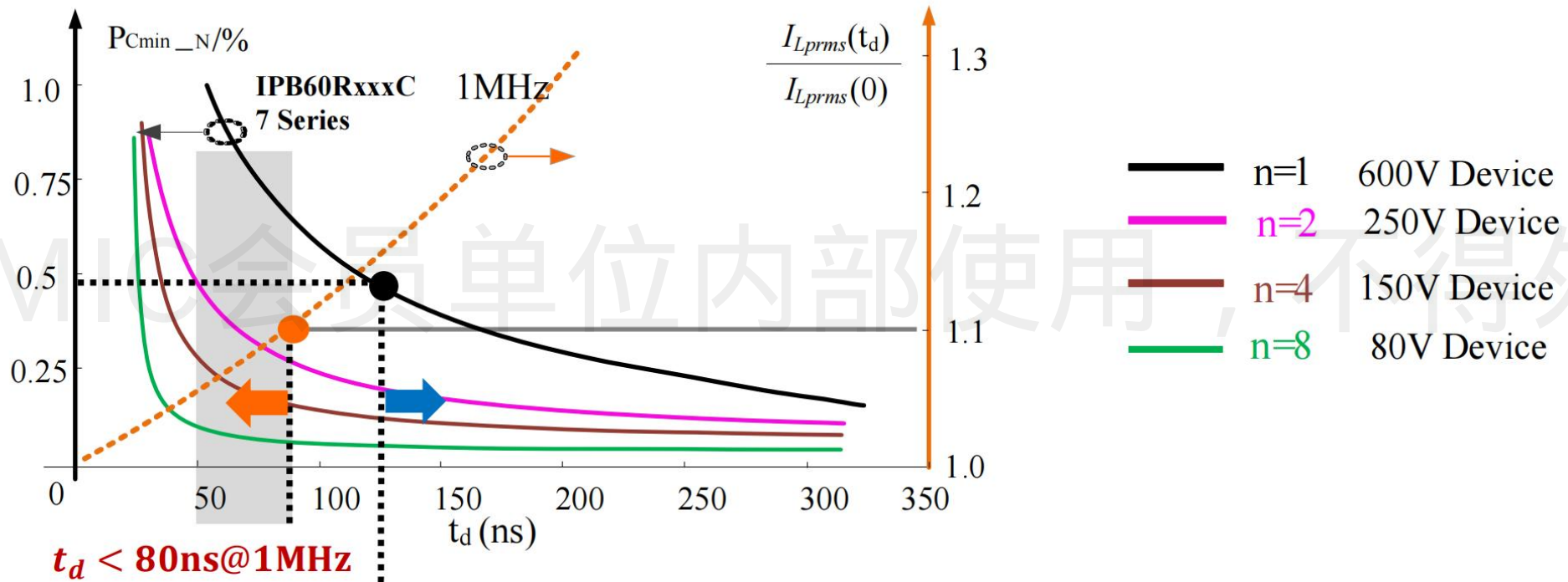
$$P_{Cmin_N} = \frac{P_{Cmin}}{P_o} = \frac{2\pi * \eta * \text{NFoM}}{t_d}$$



98% efficiency is available with Low Voltage Si devices at MHz.