



Active Dynamic Current Balancing Method for Parallel-Connected SiC MOSFETs in EV Applications

By: Junming Zhang

Zhejiang University

zhangjm@zju.edu.cn

Aug. 29, 2024

For PCIM Asia 2024, Shenzhen

联盟内部资料 请勿外传



Contents

- 1. Background**
- 2. Challenges and Solutions**
- 3. Active Gate Drive (AGD) method**
- 4. Experimental Results**
- 5. Conclusion**

联盟内部资料 请勿外传

1. Background

■ SiC MOSFET in EV applications: replace IGBT for higher efficiency

- Limited by yield and cost, parallel operation of SiC MOSFETs is necessary

1200V/13mΩ/153A (Cree, TO-247-4), **1200V/13mΩ/160A** (Cree, Bare Die)


EV



Traction Inv.



OBC/Charger

 


~5% Energy Efficiency Improvement


联盟内部资料 请勿外传

1. Background


■ Parallel operation of SiC devices:

 

 Cree Wolfspeed 1.2kV/400A XM3 half bridge SiC MOSFET module: **4 paralleled dies**



 
IPT system of ETH: **3 paralleled discrete devices** in half bridge topology^[1] Tesla Model 3: **4 paralleled devices** in 6 half bridges^[2]



[1] R. Bosshard and J. W. Kolar, "All-SiC 9.5 kW/dm³ On-Board Power Electronics for 50 kW/85 kHz Automotive IPT System," in IEEE JESTPE, March 2017.
 [2] About the SiC MOSFETs Modules in Tesla Model 3, 2021. Available: <https://www.pntrpower.com/tesla-model3-powered-by-st-microelectronics-sic-mosfets/>

1. Background

Device lifetime

 


Current imbalance




Uneven thermal distribution



Mismatched device lifetime

 

Reliability

 



Current imbalance



Circulating current



Gate oscillation

  



1. Background

■ Factors affecting current balance:

device parameters, circuit parameters, gate driver, temperature

Type	Parameters	
Device parameters	R_{dson}	Static
	$R_{g(int)}$	Dynamic
	g_m	Dynamic
	V_{th}	Dynamic
	C_{gs}	Dynamic
Circuit parameters	L_d	Both
	L_s	Both
Gate Driver	$R_{g(ext)}$	Dynamic
	V_g	Both
Junction Temp.	T_j	Both

联盟内部资料 请勿外传


- Static current balancing is mostly related to steady state current
- Dynamic current balancing is more difficult for paralleled devices



 1. Background

■ Devices Parameters tolerance:

key point for dynamic current balancing: turn on delay & di/dt



$$i_d = g_m \cdot (V_{gs} - V_{th}) = \beta \cdot (V_{gs} - V_{th})^2$$

$$\Rightarrow \Delta i_d(\Delta V_{th}) = \frac{\partial i_d}{\partial V_{th}} \cdot \Delta V_{th} = -2\beta \cdot (V_{gs} - V_{th}) \cdot \Delta V_{th}$$

$$\Rightarrow \Delta i_d(\Delta g_m) = \frac{\partial i_d}{\partial g_m} \cdot \Delta g_m = (V_{gs} - V_{th}) \cdot \Delta g_m$$

Dynamic Current imbalance mechanism


- V_{th} & g_m : the larger the difference, the larger the current difference
- V_{th} : turn on delay & di/dt
- g_m : di/dt only
- Most device parameters tolerance affect both delay & di/dt
- Gate driver: usually has very small mismatch & tolerance

联盟内部资料 请勿外传

1. Background

■ Circuit parasitic parameters: L_s 、 L_d

➤ Source inductance L_s :

 


无Kelvin源极

$$v_{gs1} - v_{gs2} = v_{Ls2} - v_{Ls1} = L_{s2} \frac{di_{d2}}{dt} - L_{s1} \frac{di_{d1}}{dt}$$



$$v_{gs1} < v_{gs2}$$
 
$$\frac{di_{d1}}{dt} > \frac{di_{d2}}{dt}$$



Kelvin Source

- Larger L_s difference – larger current imbalance (gate circulating current)
- The faster the switching speed, the greater the impact

- Drain inductance L_d has limited effect

联盟内部资料 请勿外传



Contents


1. Background
- 2. Challenges & Solutions**
3. Active Gate Drive (AGD) Method
4. Experimental Results
5. Conclusion

联盟内部资料 请勿外传



 2. Challenges & Solutions

■ Existing Dynamic Current Balancing Methods





联盟内部资料 请勿外传




  2. Challenges & Solutions


■ Device Screening: V_{th} , g_m (Transfer Curves), time-related



 - Transfer curves of 30 devices
- SiC MOSFETs with larger dispersion



Differences almost not changed

 


- Parameters vary with temperature but differences keep almost same
- Choose devices according to current sharing requirements
- Better current sharing with larger source inductances L_s



 2. Challenges & Solutions

■ Influences of power loop parasitics: source inductances L_s



If L_{S1} and L_{S2} are different, a circulating current flows through the gate loop (loop in the figure), and lead to gate voltage difference:


$$R_g C_{gs} \frac{d\Delta v_{gs}}{dt} + \Delta v_{gs} = L_{S2} \frac{di_{D2}}{dt} - L_{S1} \frac{di_{D1}}{dt} \quad (\Delta v_{gs} = v_{gs1} - v_{gs2})$$

$$i_{Di} = K(v_{gsi} - V_{th})^2$$


Different source potentials charge C_{gs} , and lead to **dynamic current imbalance**.

 2. Challenges & Solutions



■ Layout optimization of power module: **symmetry**


 
$$L_{s1} = L_{s2} = L_{s3} = L_{s4} = L_s$$



 
 
$$L_{s1} \neq L_{s2} \neq L_{s3} \neq L_{s4}$$



联盟内部资料 请勿外传

  2. Challenges & Solutions




■ Coupled drain inductors: **DMC (Differential Mode Choke)**




- Force currents in two coils to be equal based on magnetic coupling
- Simple but bulky size
- Large number of DMCs for multiple paralleled devices

   2. Challenges & Solutions


■ Coupled source inductor: **CMC (Common mode choke)**




Coupled source inductor (air core)

 

DM equivalent circuit

 

CM equivalent circuit

 

Coupled source inductor (w/ core)

- Large L_s benefit current balancing
- Large L_s cause high voltage spike
- Coupled L_s : combined



The figure illustrates a turn-on time and current slew detection circuit. On the left, a timing diagram shows the relationship between drain current I_D , source voltage V_{SS} , output voltage V_O , and gate voltages V_{CP1} and V_{CP2} over time t . The output voltage V_O shows a transient during turn-on, with V_{O1} and V_{O2} marking the start and end of the slew. The gate voltages V_{CP1} and V_{CP2} show corresponding transitions with delays Δt_{ax} and Δt_{bx} .

The main circuit schematic includes a SiC MOSFET model with parameters L_D , C_{GD} , C_{GS} , C_{DS} , L_S , and L_{SS} . The circuit is divided into five numbered blocks: 1) A +5V reference and buffer; 2) A CPLD; 3) A +20V and +5V reference and buffer; 4) A differential amplifier with two op-amps U_1 and U_2 ; and 5) A differential amplifier with two op-amps B_1 and B_2 . The circuit also includes a current source I_D and a load inductor L_S . A yellow box at the bottom states "Turn-on time and current slew detection". A blue box on the right contains the equation $V_{ss} = L_s \cdot di/dt$ and the text "Ids reconstruct".

-



2. Challenges & Solutions

■ Summary of state-of-the-art methods

➤ **Device Screening:**

costly & low efficiency (parameters are temp. & time depended)

Still affected by **circuit parasitic parameters**

➤ **Layout optimization:**

need device screening to achieve good current balancing

➤ **Coupled inductors:**

Bulky & introduce high parasitics (extra voltage stress)

➤ **Active gate Driver:**

high complexity (analog & digital circuit)

low response time (multiple cycles)

联盟内部资料 请勿外传



Contents

1. Background
2. Challenges & Solutions
- 3. Active Gate Drive (AGD) Method**
4. Experimental Results
5. Conclusion

联盟内部资料 请勿外传

3. AGD Method

■ Active gate driver

 


Diagram of active gate driver

To achieve real-time dynamic current control (in single switching cycle):


- High-bandwidth current detection (**more than 10~30MHz**)
- Low delay time of control loop (**ns level**)
- Flexibility & scalability (**easily extended for multiple devices**)
- Simple, low cost & easy for integration

联盟内部资料 请勿外传



3. AGD Method


■ Proposed active gate driver method

 

Voltage Controller Current Source:

VCCS1: source current to gate

VCCS2: sink current to gate

 

Current sensing: L_s (Kelvin source
& Power source)


Turn on point & di/dt (amplitude)

联盟内部资料 请勿外传




3. AGD Method

■ VCCS Implementation

 


Current Sink Circuit


BJT only
(V_{Ls} is large)

 
 
$$I_{\text{sink}} = \frac{v_{Ls2} - v_{Ls1} - V_{BE,T}}{R_1}$$



Current Source Circuit

 


$$I_{\text{source}} = \frac{v_{Ls1} - v_{Ls2} - V_{BE,T}}{R_2}$$

联盟内部资料 请勿外传

3. AGD Method

■ Principle of Operation

 

➤ di/dt detection:

$$v_{Lsi} = L_s \frac{di_{di}}{dt}$$

➤ VCCS (Voltage Controlled Current Source)

- $v_{Ls1} > v_{Ls2}$: I_{source} is injected to i_{g2}
- $v_{Ls1} < v_{Ls2}$: I_{sink} is extracted from i_{g2}

✓ No complex current detection


✓ No high BW OPA required

联盟内部资料 请勿外传



3. AGD Method

■ Principle of Operation

 

Take turn-on transient as an example

Assuming V_{gs} of device 1 reaches V_{th} firstly

Stage 1 ($t_0 \sim t_1$):

V_{gs} below V_{th} , currents keep at 0


联盟内部资料 请勿外传

x: parameters without AGD
x': parameters with AGD



3. AGD Method

■ Principle of Operation

 

x: parameters without AGD
x': parameters with AGD

Take turn-on transient as an example

Assuming Vgs of device 1 reaches Vth firstly

Stage 1 ($t_0 \sim t_1$):

Vgs below Vth, currents keep at 0

Stage 2 ($t_1 \sim t_2$):


Device 2 reaches Vth firstly, $V_{Ls2} > V_{Ls1}$, I_{sink} sinks current from Vgs2, di/dt reduced.

联盟内部资料 请勿外传



3. AGD Method

■ Principle of Operation

 

x: parameters without AGD
x': parameters with AGD

Take turn-on transient as an example

Assuming V_{gs} of device 1 reaches V_{th} firstly

Stage 1 ($t_0 \sim t_1$):

V_{gs} below V_{th} , currents keep at 0

Stage 2 ($t_1 \sim t_2$):

Device 2 reaches V_{th} firstly, $V_{Ls2} > V_{Ls1}$, I_{sink} sinks current from V_{gs2} , di/dt reduced.

Stage 3' ($t_2 \sim t_3'$):

Device 1 reaches V_{th} at t_2 , current rising.


If $di/dt(2) \neq di/dt(1)$, VCCS will source/sink current from Device 2 to keep same di/dt

联盟内部资料 请勿外传




 3. Operation Principle of Proposed AGD

■ Scalability for multiple paralleled devices



Daisy-chain structure

 



Master-slave structure

联盟内部资料 请勿外传

  3. Operation Principle of Proposed AGD

■ Control scheme 1: democracy master-slave

The determination of master device: automatic





Using AND/OR gate, the slowest/fastest device is automatically selected as reference

- Feedback circuit is simplified (only sink or source is required)
- The voltage drop of AND/OR gate will affect the current balancing accuracy

  3. Operation Principle of Proposed AGD

■ Control scheme 2: dedicated master-slave

The determination of master device: dedicated




Any device can be chosen as the master device

- Both sink and source current is required
- No extra circuit for master device selection

 3. Operation Principle of Proposed AGD

■ Control scheme 3: average method

The determination of master device: average



the average di/dt is used as the reference with a resistor network

联盟内部资料 请勿外传

- Both sink and source current is required
- No voltage drop causing voltage balancing accuracy




Contents

1. Background
2. Challenges & Solutions
3. Active Gate Drive (AGD) Method
- 4. Experimental Results**
5. Conclusion


联盟内部资料 请勿外传

4. Experimental Results

■ Experimental platform

 

DPT (double pulse test) circuit

 




Hardware platform

Components	Parameters
T_1, T_2 (NPN, CPH3215)	30V/3A/500MHz
T_3, T_4 (PNP, CPH3115)	30V/3A/450MHz
R_1, R_2	1Ω
SiC MOSFET (C3M0032120K)	1.2kV/63A/32mΩ


联盟内部资料 请勿外传

4. Experimental Results

■ Response time of VCCSs

   

VCCS (sink): **~4ns**

 


VCCS (source): **~7ns**


联盟内部资料 请勿外传

4. Experimental Results


■ 6pcs parallel example:

 


6*C3M0032120K

 

Dedicated master-slave structure

 

PCB Layout

 



Schematic





4. Experimental Results

■ Experimental waveforms: 2pcs parallel

CGD

  

AGD

  

Eon: ~37% improvement

CGD: 509/512uJ, 13.8%

AGD: 578/631uJ, 8.8%

Eoff: ~75% improvement

CGD: 233/414uJ, 56%



AGD: 211/246uJ, 13.8%

联盟内部资料 请勿外传



4. Experimental Results

■ Experimental waveforms:

CGD

  

AGD

  


Dynamic current sharing performance: ~50% improvement



4. Experimental Results

■ Experimental waveforms:

 

Turn on loss deviation: **~55% improvement**

		Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	$\sigma\%$
CGD	Turn-on (μJ)	591	749	703	503	451	418	21.8%
	Turn-off (μJ)	311	226	241	353	297	244	16.1%
AGD	Turn-on (μJ)	478	581	559	456	447	428	11.8%
	Turn-off (μJ)	283	302	293	357	311	291	7.8%

standard deviation: **~50% improvement**



Contents

1. Background
2. Challenges & Solutions
3. Active Gate Drive (AGD) Method
4. Experimental Results
- 5. Conclusion**

联盟内部资料 请勿外传



5. Conclusion

- Parallel operation of SiC MOSFET is very common for high power applications (die, discrete, even power module)
- SiC devices have large parameters tolerance, some of them is temperature & time depended (device screen cannot guarantee a good match in the lifetime & operation conditions)
- Circuit parasitic also affect current balancing of paralleled devices
- Active gate drive is a promising way for dynamic current balancing

联盟内部资料 请勿外传



Thank you!

联盟内部资料 请勿外传